
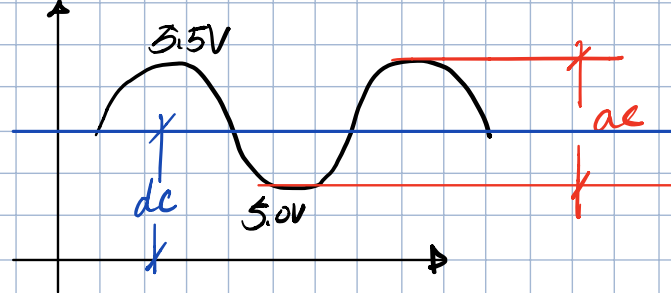


# Small Signal diode model.

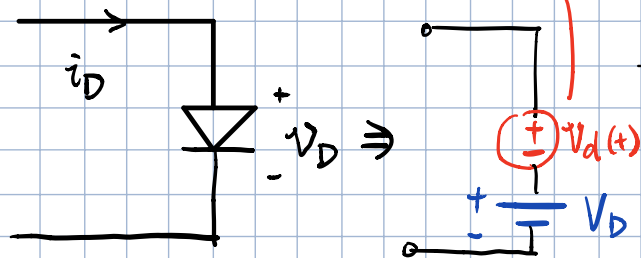


$$DC: V_D, I_D$$

upper-case

$$ac: v_d, i_d$$

lower-case

$$total: (DC+ac) v_D, i_D$$

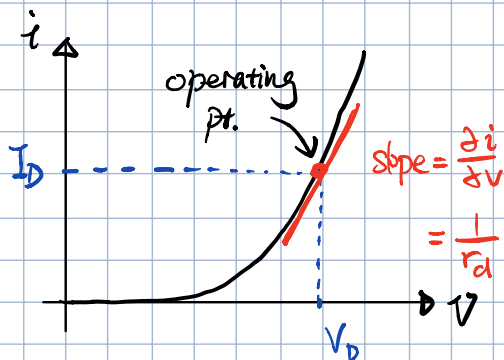

$I_D$ : diode DC current

$$i_D(t) = I_S e^{v_D/V_T}$$

$$v_D = V_D + v_d$$

$$i_D(t) = I_S e^{(V_D + v_d)/V_T}$$

$$= I_S e^{V_D/V_T} \cdot e^{v_d/V_T}$$

$$= I_D \cdot e^{v_d/V_T}$$

assume  $\frac{v_d}{V_T} \ll 1 \Rightarrow$



$$\approx I_D (1 + \frac{v_d}{V_T})$$

$$\approx \underbrace{I_D}_{DC \text{ component}} + \underbrace{\frac{I_D}{V_T} v_d}_{ac \text{ component}}$$



$$\approx I_D + \frac{1}{r_d} v_d$$

$$\frac{I_D}{V_T} = \frac{1}{r_d}$$

Small-signal model  
(only ac component)

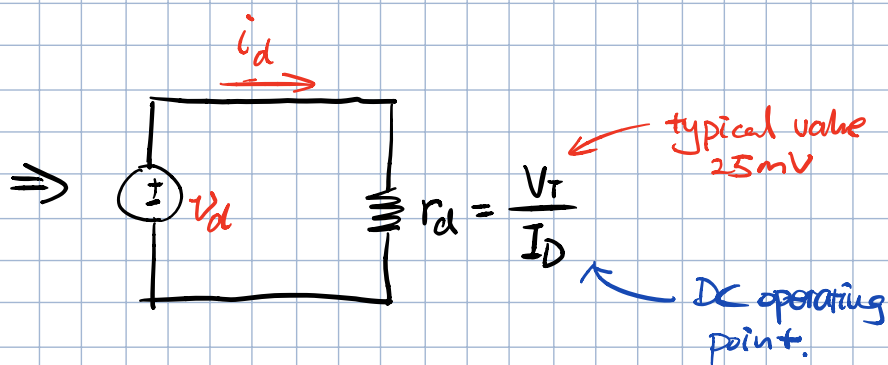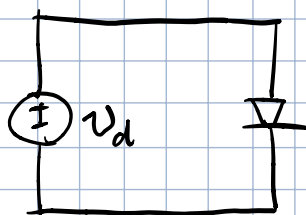

## Example 1

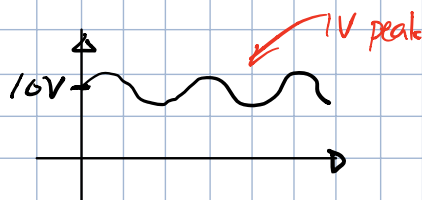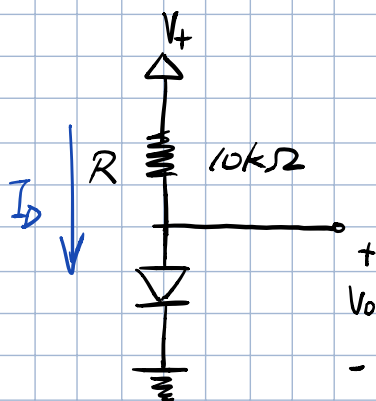

the diode has 0.7V at 1mA.

Step (1): find the DC operating point ( $I_D, V_D$ )

$$I_D = \frac{10V - 0.7V}{10k\Omega} = 0.93mA$$


(very close to 1mA, don't use more iteration)

DC operating pt is (0.93mA, 0.7V)

Step (2): use the DC operating pt to calculate  $r_d$


$$r_d = \frac{V_T}{I_D} = \frac{25mV}{0.93mA} = 26.9\Omega$$

## Small signal model.

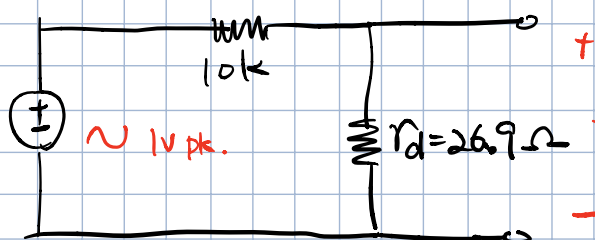

$$v_d = \frac{r_d}{R + r_d} \times 1V_{pk} = 2.68mV$$

overall voltage across the diode.

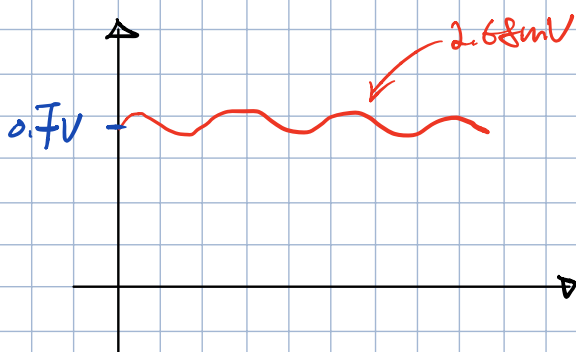


$$V_D = V_D + v_d$$

0.7V      ac comp. (2.68mV)

diode is a good regulator! (compare 1V oscillation of 10V  
 $\frac{1}{10} \approx 2.68mV$  oscillation of 0.7V)

## example 2.



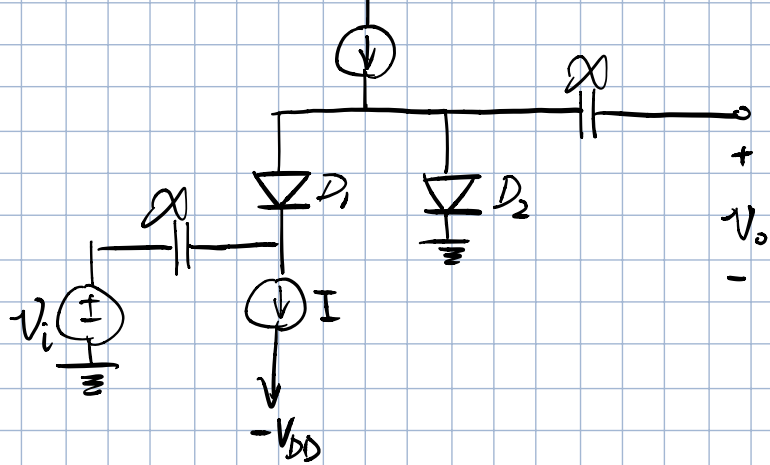


{ find  $\frac{v_o}{v_i}$  }

① find DC operating pt.

② find  $r_{d1}$  &  $r_{d2}$

③ find  $\frac{v_o}{v_i}$

{ DC circuit }

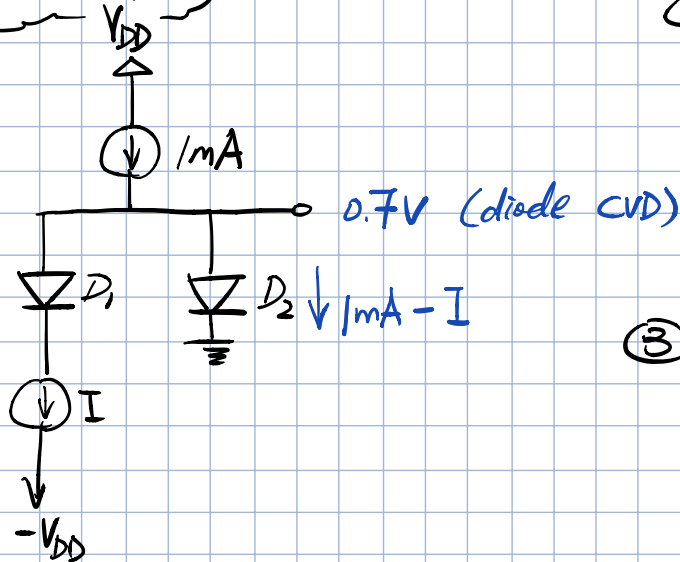


②

$$r_{d1} = \frac{V_T}{I}$$

$$r_{d2} = \frac{V_T}{I-I}$$

③ small-signal model

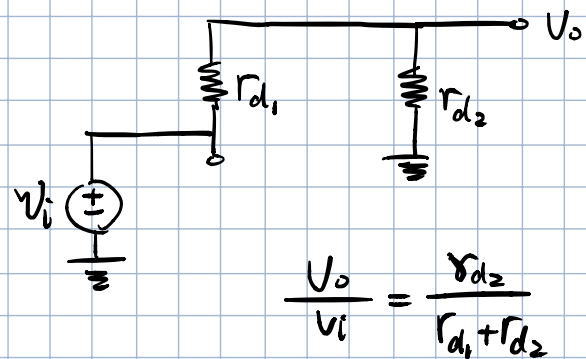

$$\frac{v_o}{v_i} = \frac{r_{d2}}{r_{d1} + r_{d2}}$$

$$= \frac{V_T / (I-I)}{V_T / I + V_T / (I-I)}$$

gain is controlled by I  
i.e.  $I = 0.5 \text{ mA}$   
gain =  $\frac{1}{2}$

$$= \frac{I}{I} \left( \frac{V}{V} \right)$$