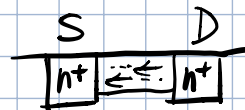




- 1) raising V_{GS} beyond V_{th} causes a channel (e^-) to form between S & D
channel depend $\propto V_{ov}$

$$V_{ov} = V_{GS} - V_{th}$$

- 2) Increasing V_{DS} a little causes current to flow from D to S.




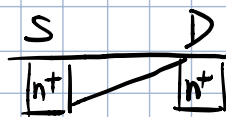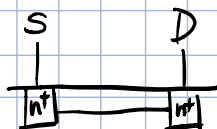- 3) Increasing V_{DS} much more causes the channel to taper at the drain when $V_{DS} = V_{ov} = V_{GS} - V_{th}$ the channel at the drain is pinched off.





current saturator.

NMOS





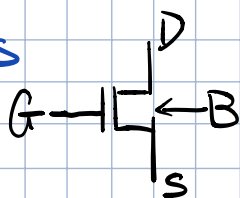


$$r_{DS} = \frac{1}{k_n' \left(\frac{W}{L}\right) V_{ov}}$$

"channel persistence"

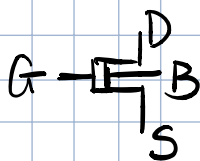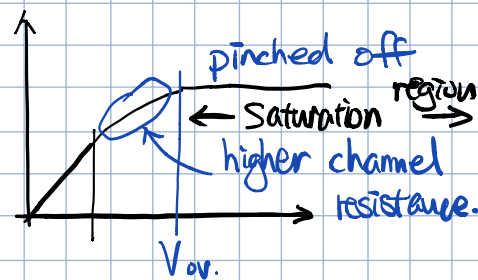

PMOS

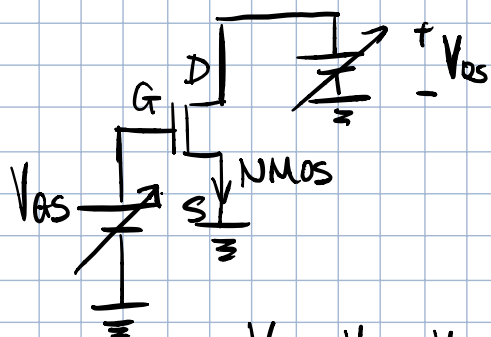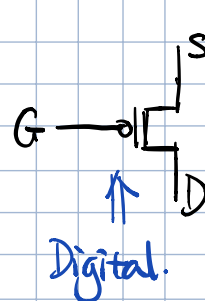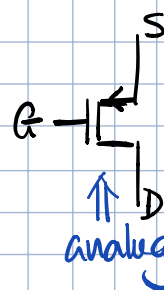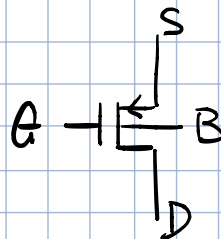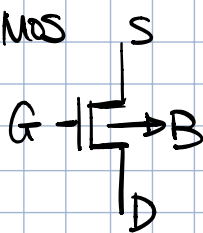


$$V_{ov} = V_{GS} - V_{th}$$

$V_{th} > 0$ threshold.



$$V_{ov} = V_{GS} - V_{th}$$

$$k_n' = \mu_n C_{oxide}$$

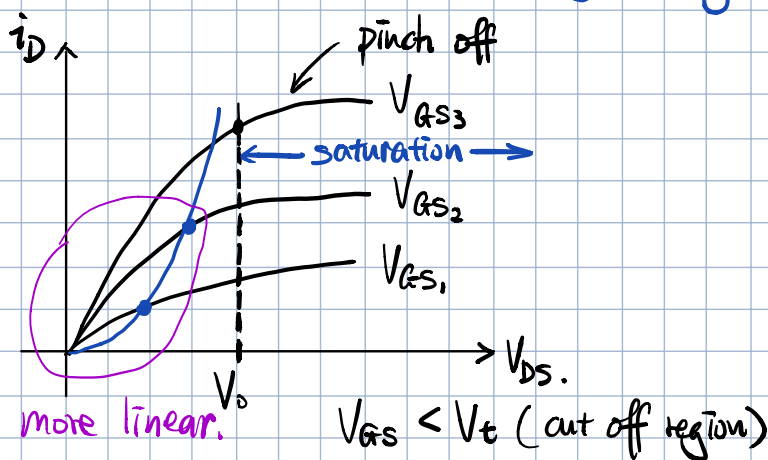

triode region: $i_D = k_n' \left(\frac{W}{L}\right) (V_{ov} V_{DS} - \frac{1}{2} V_{DS}^2)$

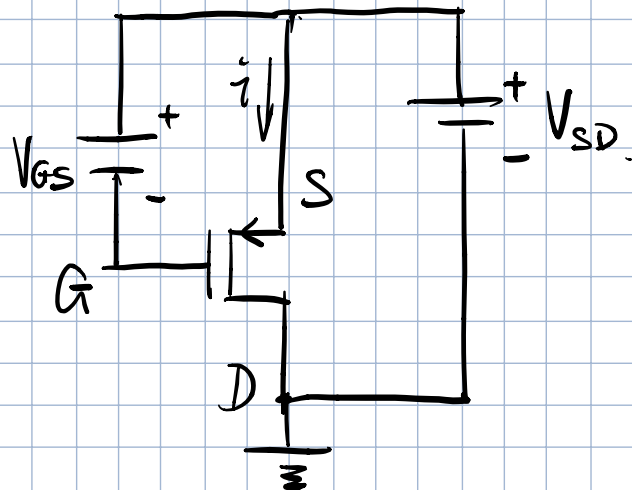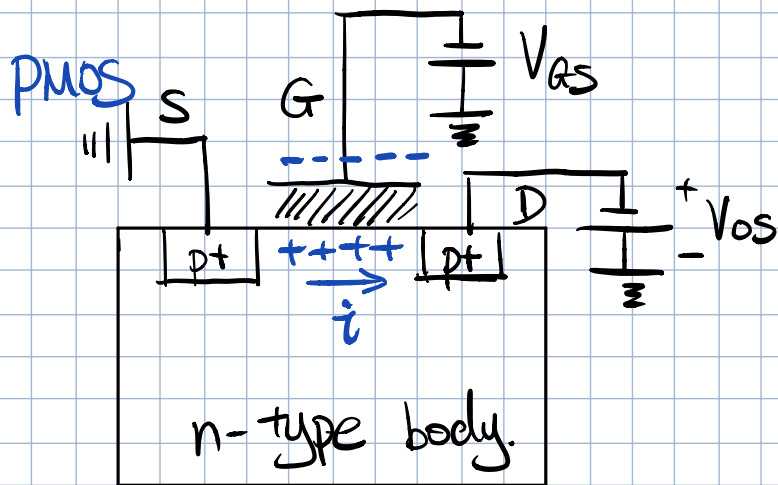saturation: $i_D = k_n' \left(\frac{W}{L}\right) V_{ov}^2$



$V_{th} < 0$ (threshold)

$|V_{ov}| = |V_{GS}| - |V_{th}|$



$k'_p = \mu_p C_{ox}$

triode region:

$i_D = k'_p \left(\frac{W}{L}\right) (|V_{ov}| |V_{DS}| - \frac{1}{2} V_{DS}^2)$

$i_D = \frac{1}{2} k'_p \left(\frac{W}{L}\right) V_{ov}^2$

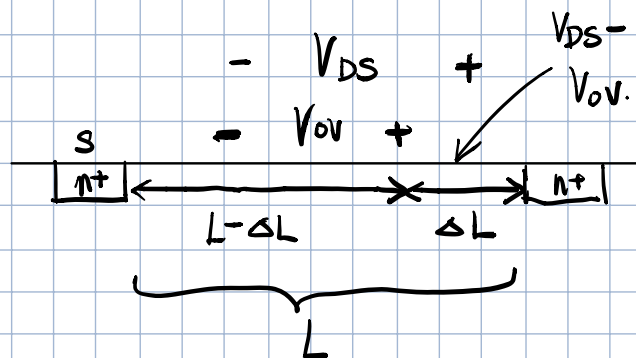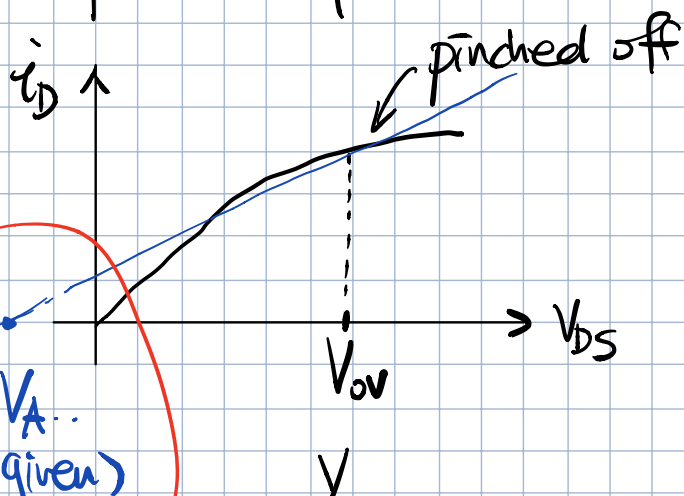→ finite output resistance in saturation.



V_A : early voltage. large negative value.

$i_D = k'_p \left(\frac{W}{L}\right) V_{ov}^2 \left(1 + \frac{V_{DS}}{V_A}\right)$

$$I_D = \frac{1}{2} k_n \left(\frac{W}{L} \right) V_{ov}^2 (1 + \lambda V_{DS})$$

saturation current w/o channel length modulation. $\parallel 1/V_A$

$$1/r_o = dI_D/dV_{DS} = \frac{1}{2} k_n' \left(\frac{W}{L} \right) V_{ov}^2 \lambda = I_D \lambda, \quad r_o = \frac{1}{I_D \lambda} = \frac{V_A}{I_D}$$

model NMOS in saturation. $V_{ov} = V_{GS} - V_t$

