 



Storage Element.

Latch



clk	D	Q
0	0	0/1
0	1	0/1
1	0	0
1	1	1


prev. stored value.

 

operation = if $clk=1$, $Q=D$, But when $clk=0$, the feedback loop stores the value that D was when clk was 1.


Flip-Flop :

 circuit that stores a value on the edge of a clock signal.




clk	Q
0	0/1
1	0/1
1	D

stored value

 

Timing Diagram.

 

Note: We do not need to look at Q_m to draw the waveform for Q s because the FF simply stores the value of D at the movement when clock


Flip-Flop w/ Enable.

if $E=0$, Q can't change.






if $E=1$, the flip-flop works normally.

 

N-bit register.

 


- comprises n FFs in parallel.

- if $E=1$, when on \neg clock edge, store the n -bit value of D in the register.

- if $E=0$, the data cannot change.

n-bit counter.

 

- if $R=0$, then on an \neg clock $Q=0$


- if $E=1$,

if $L=1$, then on \neg clock edge, $Q=D$

else if $L=0$, then on \neg clock edge, $Q=Q+1$

Else if $E=0$,

Q cannot change.

 

Verilog.

```
module counter (L, E, R, D, clock, Q);
```

```
parameter n=16;
```

```
input L, E, R, clock;
```

```
input [n-1:0] D;
```

output reg. [n-1:0] Q;

always @ (posedge clock)

if (R==0) Q<=0;

else if (E==1)

if (L==1) Q<=D;

else Q<=Q+1;

endmodule.

use <= for FFs
use = otherwise.
(non-blocking vs.
blocking assign.)

Design Example:


A factory bakes cookies that move down a conveyor belt. There are 3 sensors examine each cookie:

S₀: gives 1 iff a cookie is burned.

S₁: gives 1 iff a cookie is too light in weight.

S₂: gives 1 iff a cookie is not round.

 - A logic function $R=1$ rejects only cookie for which two or more sensors produce 1. Cookies not rejected get wrapped.



- Design a finite state machine (controller) that does the following. synchronized. by a clock signal: