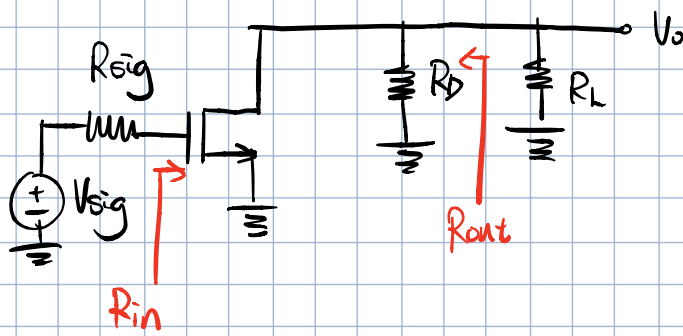



Single transistor Amplifier. comparison.




{CS/CE amplifier.}

- high R_{in}
- high voltage gain.
- moderate R_{out}

{CS/CE with R_S/R_E amplifier.}

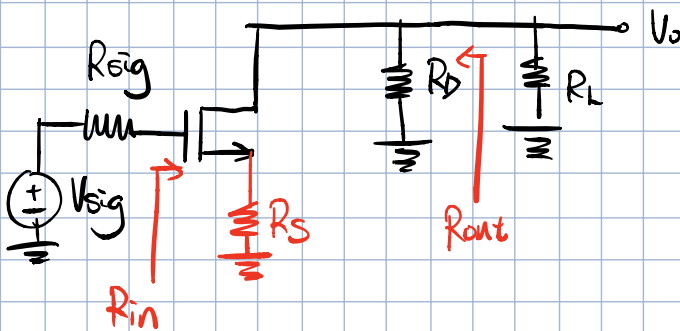


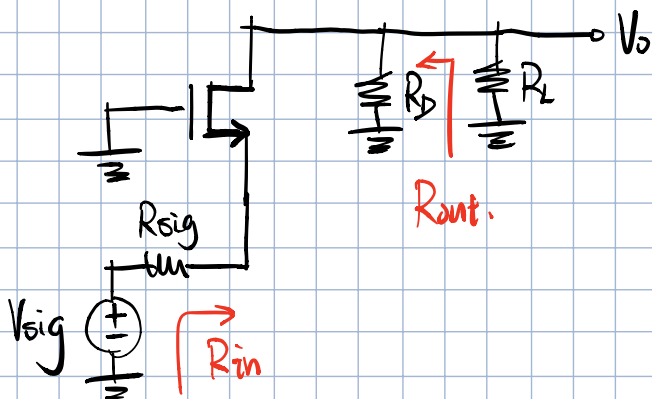- high R_{in}
- reduced gain compare to CS/CE
- moderate R_{out}
- reduce signal distortion.
- less sensitive to device variation




{CG/CB amplifier.}

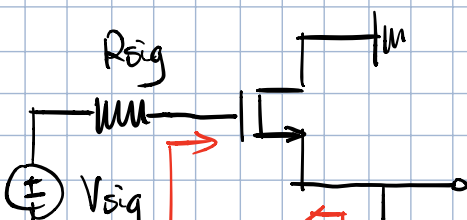- low R_{in}
- lower voltage gain compare to CS/CE
- moderate R_{out}
- limited application.





{CD/CC (source/emitter follower)}

- high R_{in}


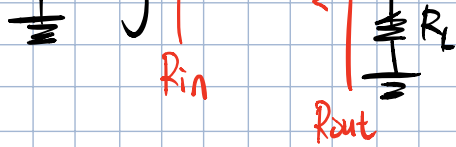


- voltage gain ≈ 1
- low R_{out}
- good buffer.

Biasing for discrete amplifier.

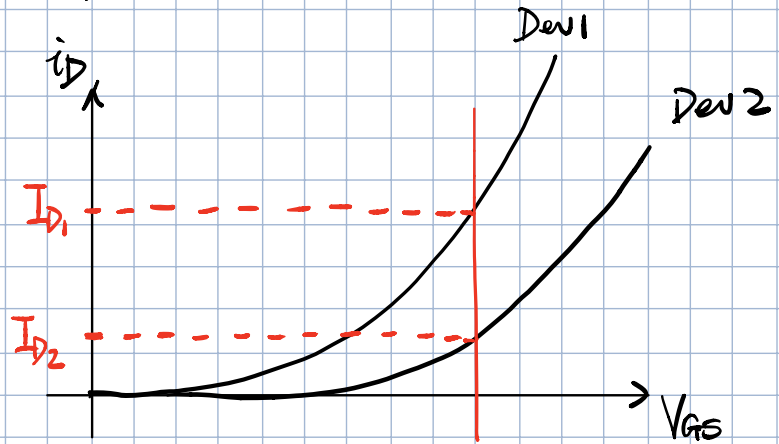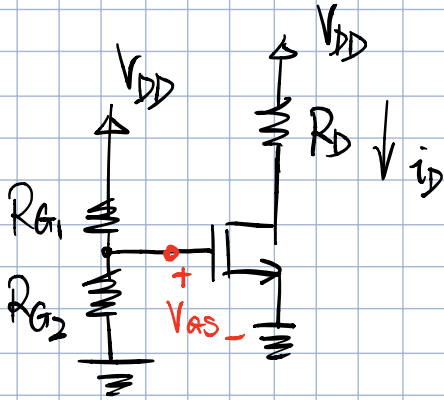


fixed V_{GS} (not good design choice)

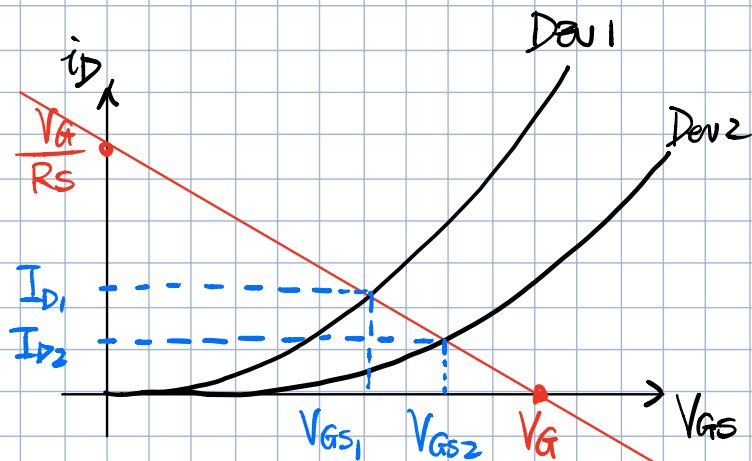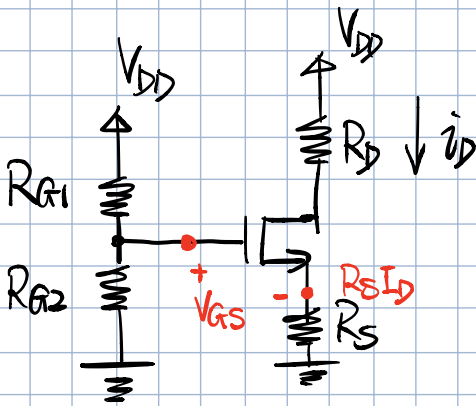


much smaller gap

$$V_{GS} = V_G - R_S I_D$$

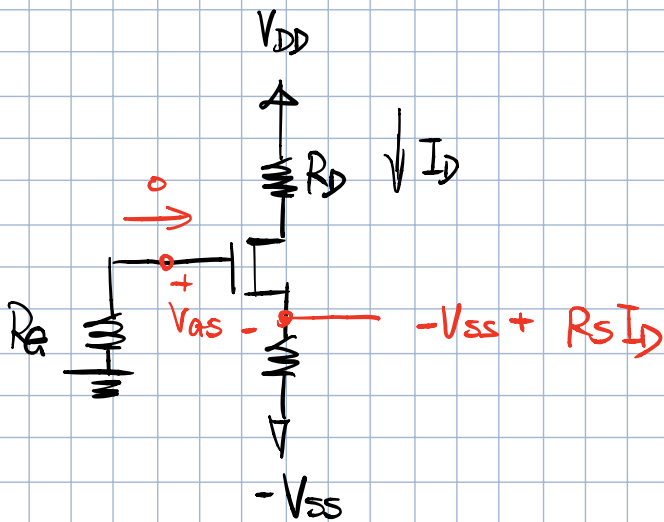


$$V_{GS} = 0 - (-V_{SS} + R_S I_D)$$

$$= V_{SS} - R_S I_D$$

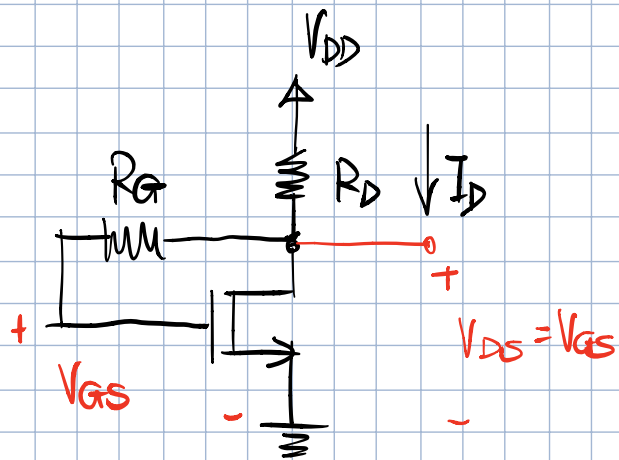

$$V_{GS} + R_D I_D = V_{DD}$$


$$V_{GS} = V_{DD} - R_D I_D$$

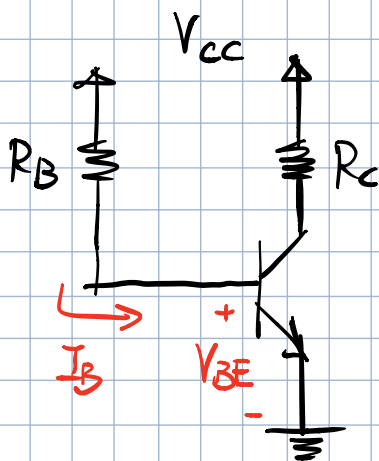


$$(V_{CC} - V_{BE}) / R_B = I_B$$

$$I_C = \beta I_B$$

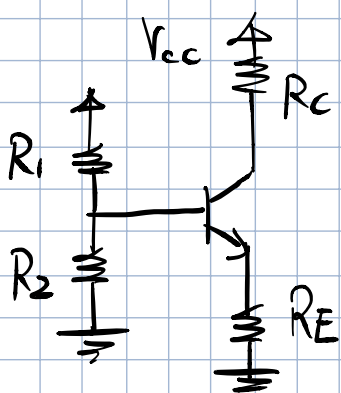→ sensitive to β value.
(not a good biasing style)



(Good Biasing example)

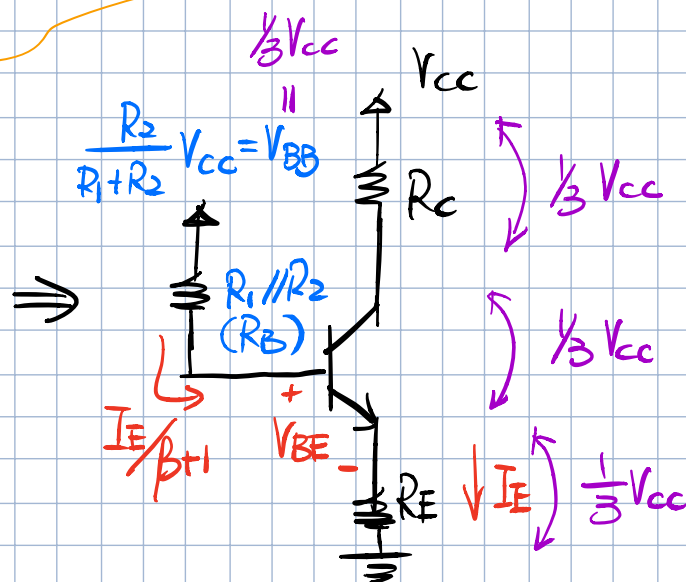

rule of thumb
of choice

$$R_E I_E + V_{BE} + R_B \frac{I_E}{\beta + 1} = V_{BB}$$

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + R_B / (\beta + 1)}$$

→ to make the design less sensitive to β value + temp.

$$V_{BB} \gg V_{BE} (\sim 0.7V)$$

$R_E \gg R_B / \beta + 1 \rightarrow$ select R_1 & R_2 , so that the
current through them is $I_E - 0.1 I_E$