
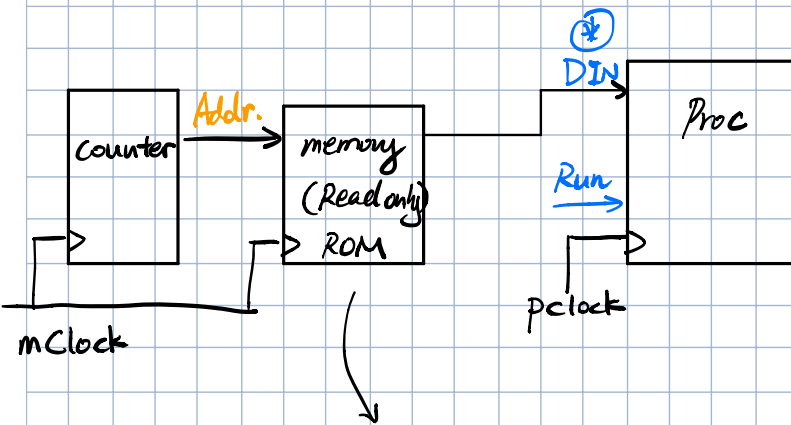


 Add an external counter & memory (Lab 1, part 2)



* usually DIN is used for Instructions.
(IIIXXXYYY) But for "mvi", DIN
is also used for the data.



* the memory that you created.
using Quartus has a register
to hold Addr. Thus, a clock
edge is needed in the memory
before it provides data.

Enhanced Processor (lab 2)

- change all registers to 16-bits.
- add an interface btw the processor and memory.
- add 2 instructions for reads/write of memory &
2 instructions for loop control.
- change R7 into a program counter (PC) register. The PC register
always holds the address in memory of the next instruction to be
executed.

New Instructions


ld rX, [rY] rX ← contents of memory using rY for the
Address.

st rX, [rY] store rX into memory at address in rY

$mvnz\ rX, rY$ $rX \leftarrow rY$ iff register $G \neq 0$

$mvnc\ rX, rY$ $rX \leftarrow rY$ iff last add/sub did not produce a carry-out.

Modified Proc.

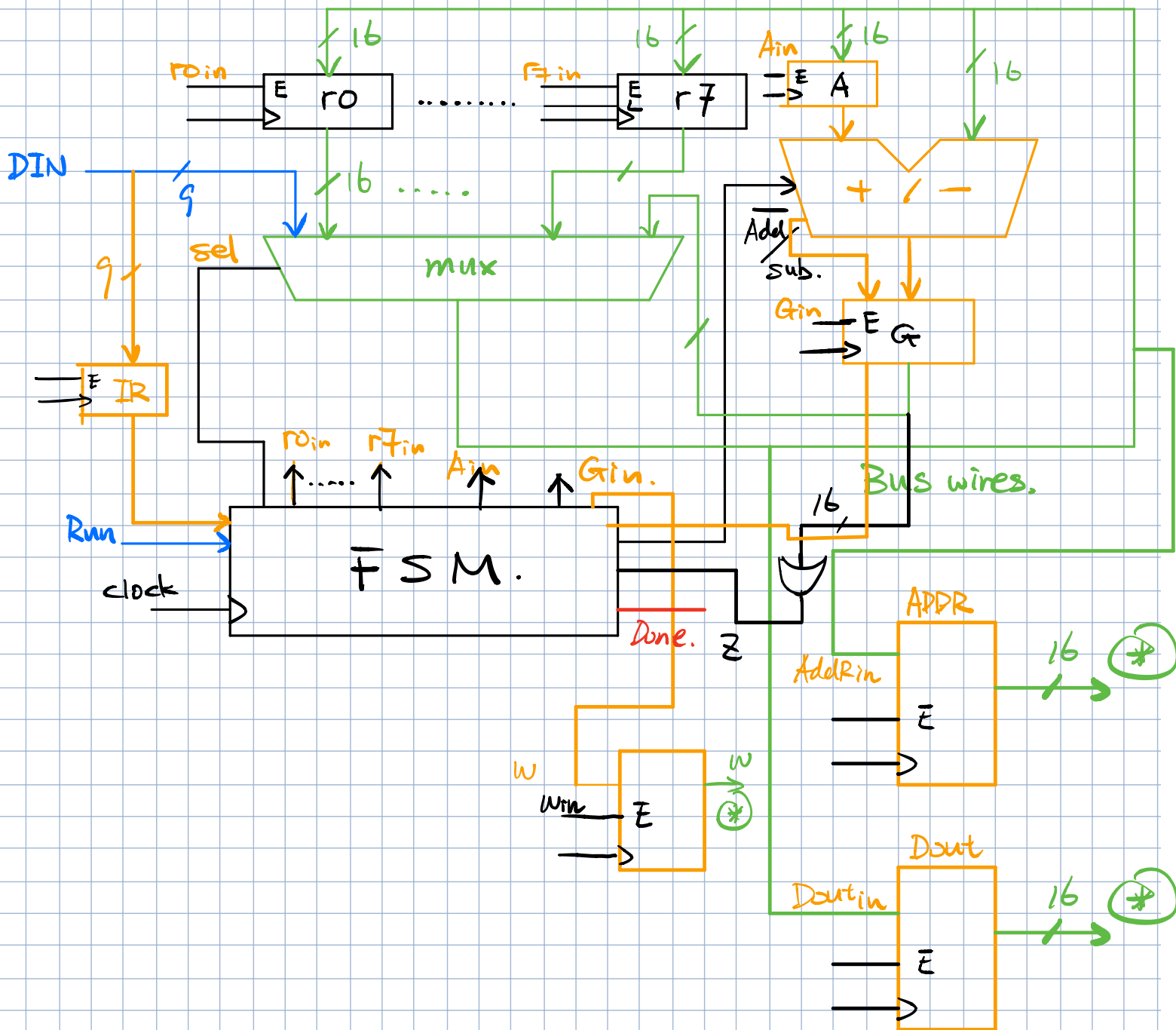

Connecting the processor to memory & Input/output devices

- Assume that the memory contains 256 words of


data (instructions)

\therefore the memory rows have addresses from 0 to 255.

In binary, 0000 0000 to 1111 1111

\therefore the memory has 8 address input. $A_7 \dots A_0$

 - Also assume there's an output port connected to some LEDs



(*) The AND gate provides address-decoding. In this case.

- memory is selected by any address w/ $A_{12} = 0$

- LED output port is selected by any address w/ $A_{12} = 1$

- using only A_{12} for address-decoding is not very flexible.

In lab 2 we use $A_{15} \dots A_{12}$ for address decoding.

