


Transmission line:

Def: A transmission line is a structure of conduction for guiding EM waves from one pt. to another

wave convey:

- ① power ex. power line
- ② signal ex. Twisted pair cabs
PCB Traces

Circuit Theory vs. Transm. line Theory:

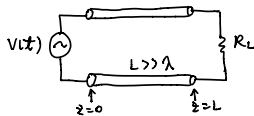

$$V(z=0) \neq V(z=L)$$


Circuit Theory:

- Assumes the dimensions of the circuit are small compared to the λ .
- For a sinusoidal source $V(z)$ does not change w z .

Trans. Line Theory:

- L is not $\ll \lambda$. rules of thumb $L > 0.1\lambda$
- magnitude & phase of $V(z)$ change w z
- KVL & KCL do NOT apply when solving Trans. line problems.

Example:

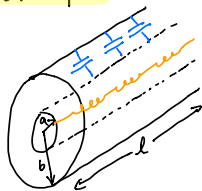

Capacitance:




$$C = \frac{2\pi\epsilon\epsilon_0}{\ln(b/a)} \text{ [F]}$$

$$C' = \frac{C}{l} = \frac{2\pi\epsilon}{\ln(b/a)} \text{ [F/m]}$$


Inductance:

$$L = \frac{\mu_0}{2\pi} \ln(b/a) \text{ [H]}$$
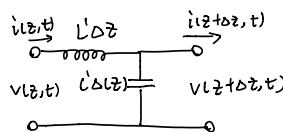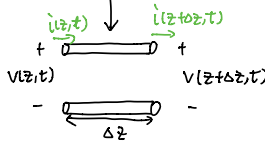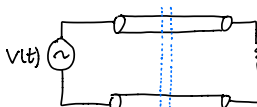
$$L' = \frac{\mu_0}{2\pi} \ln(b/a) \text{ [H/m]}$$




Losses:

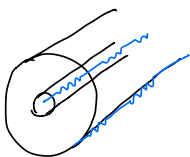

resistor
dielectrics

Complete model:

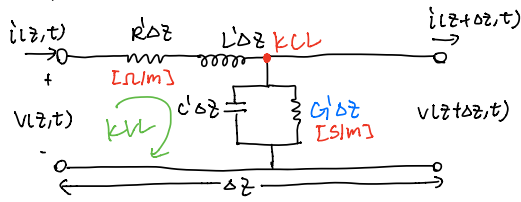

KVL: $-v(z,t) + R'\Delta z \cdot i(z,t) + L'\Delta z \frac{di(z,t)}{dt} + v(z+\Delta z,t) = 0$

$$\lim_{\Delta z \rightarrow 0} \frac{v(z+\Delta z,t) - v(z,t)}{\Delta z} = -R' i(z,t) - L' \frac{di(z,t)}{dt}$$

$$\frac{dv(z,t)}{dz} = -R' i(z,t) - L' \frac{di(z,t)}{dt} \quad (1)$$

Telegrapher's Equation

KCL: $i(z,t) - i(z+\Delta z,t) - G'\Delta z v(z+\Delta z,t) - C'\Delta z \frac{dv(z+\Delta z,t)}{dt} = 0$

$$\frac{di(z,t)}{dz} = -G' v(z,t) - C' \frac{dv(z,t)}{dt} \quad (2)$$

Oliver Heaviside

Solving Telegrapher's Equations:

- Use phasors

$$e(t) = -R i(t) - L \frac{di(t)}{dt} + \frac{1}{C} \int i dt$$

$$e(t) = E_0 \cos(\omega t)$$

$$i(t) = I_0 \cos(\omega t)$$

$$i(t) = I_0 \cos(\omega t + \phi)$$

$$= \text{Re} \{ (I_0 e^{i\phi}) \cdot e^{j\omega t} \}$$

$$= \text{Re} \{ I_s \cdot e^{j\omega t} \}$$

phasor:

$$\frac{di(t)}{dt} = \frac{d}{dt} \text{Re} \{ I_s e^{j\omega t} \}$$

$$= \text{Re} \left\{ \frac{d}{dt} (I_s e^{j\omega t}) \right\}$$

$$= \text{Re} \{ j\omega I_s e^{j\omega t} \}$$

$$\frac{di(t)}{dt} = j\omega I_s$$

$$\int i(t) dt = \int \text{Re} \{ I_s e^{j\omega t} \} dt$$

$$= \text{Re} \left[\int I_s e^{j\omega t} dt \right]$$

$$\int i(t) dt = \frac{I_s}{j\omega}$$

$$e(t) = -R i(t) - L \frac{di(t)}{dt} + \frac{1}{C} \int i dt$$

↓ phasors

$$E_s = -R I_s - L j\omega I_s + \frac{1}{j\omega C} I_s$$

$$= -(R + j\omega L - \frac{1}{j\omega C}) I_s$$