
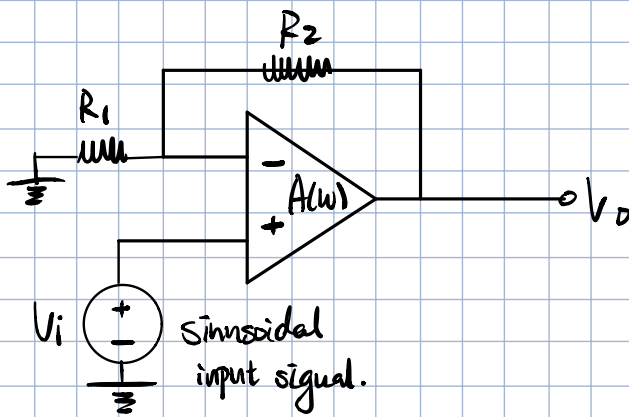


## example 1

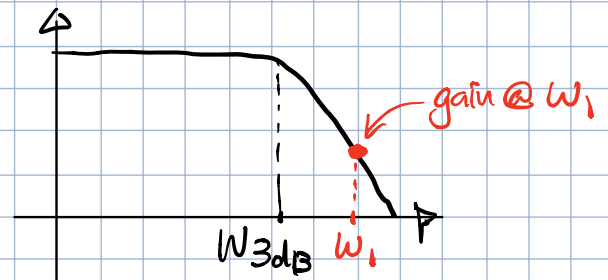

$$\frac{V_o}{V_i} = \frac{1 + \frac{R_2}{R_1}}{1 + j\omega/\omega_{3dB}}$$



to avoid SR limiting

$$SR = V_{opk} \cdot \omega$$

$$V_{opk} = \frac{SR}{\omega}$$


given

Say you have to work with  $\omega$

the input signal level will be calculated

$$V_{ipk} = \frac{V_{opk}}{\text{gain @ } \omega_1} = \frac{SR/\omega_1}{\text{gain @ } \omega_1}$$

## example

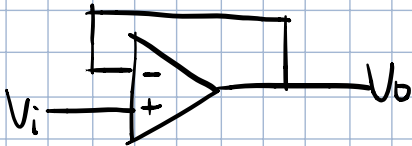


given that the Op-amp has SR of  $1V/\mu s$  and unity gain -BW product of  $1MHz$

a) find the largest possible input voltage step for which the output is not SR limited.


$$\omega_t \cdot V_{opk} = SR = 1V/\mu s = 10^6 V/s, \quad f_t = 1MHz$$

$$V_{opk} = \frac{10^6}{2\pi \times 10^6} = \frac{1}{2\pi} = 0.16V$$


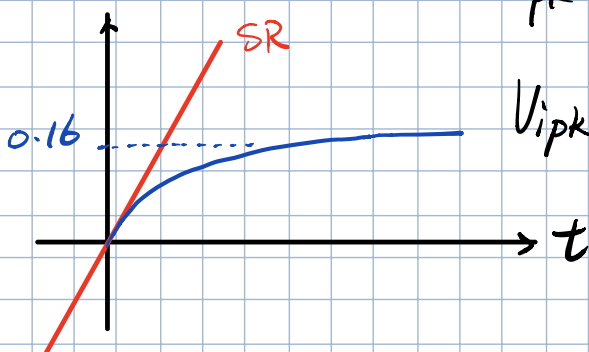
$$V_{ipk} = \frac{V_{opk}}{\text{gain}} = 0.16V$$



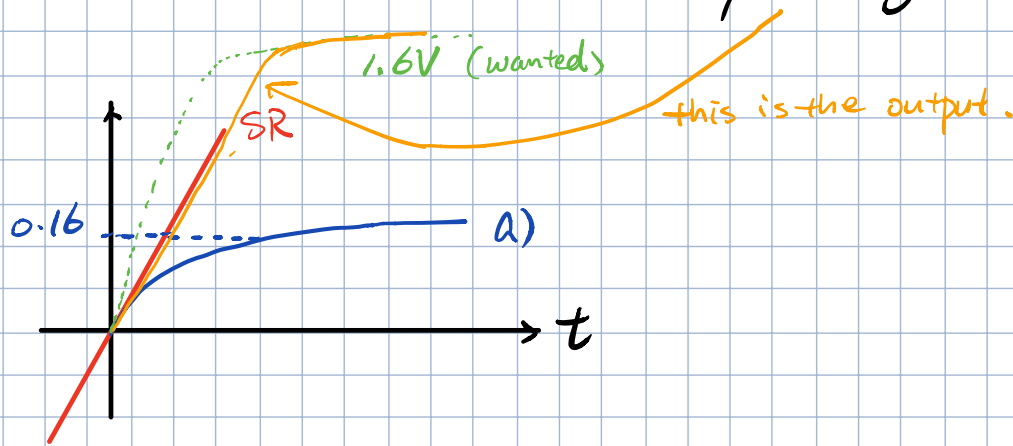b) If an input of  $10\times$  of this value in a) is used, what would be the output voltage look like?




## Semiconductor Physics.

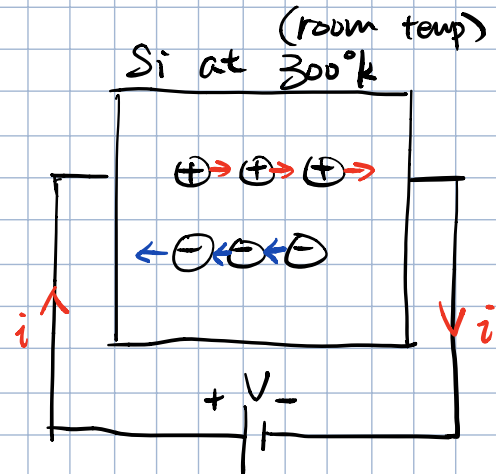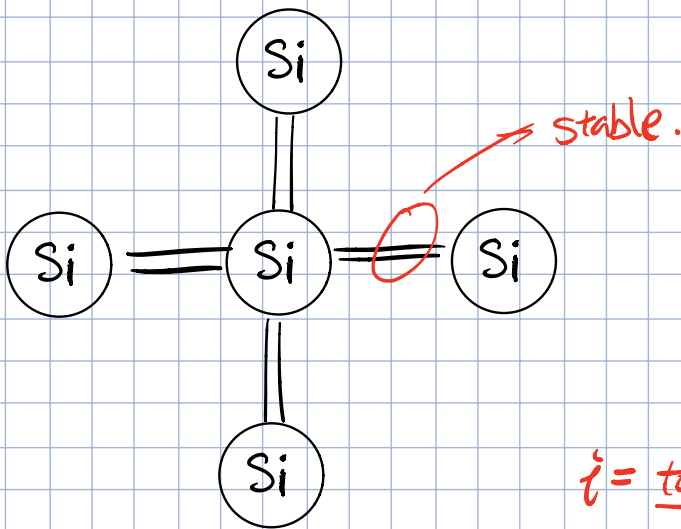


$$i = \frac{\text{total charge}}{\text{time}} = \frac{\# \text{ of holes} + \# \text{ of electrons}}{\text{time}}$$

n-type

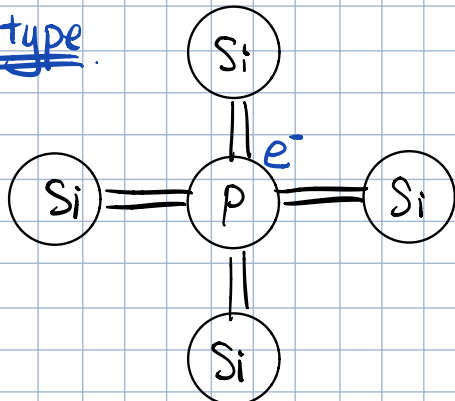


higher  $e^-$  concentration.  
(major carrier)

p-type

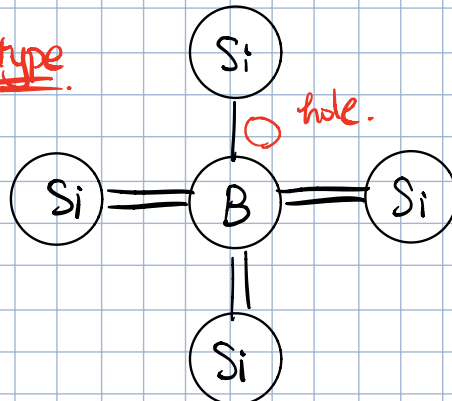

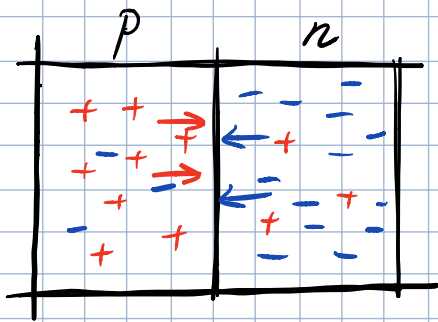
higher hole concentration.  
(major carrier)



mechanism for currents to move.

① Diffusion.

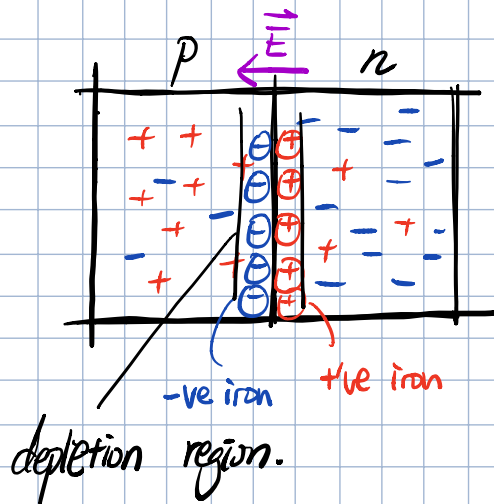higher concentration of major carriers  $\rightarrow$  lower.




② Drifting.

minority carriers are swept across the boundary by the  $\vec{E}$

① Equilibrium. (open-circuit)


$$I_{\text{Diff}} = I_{\text{Drift}} (I_s)$$
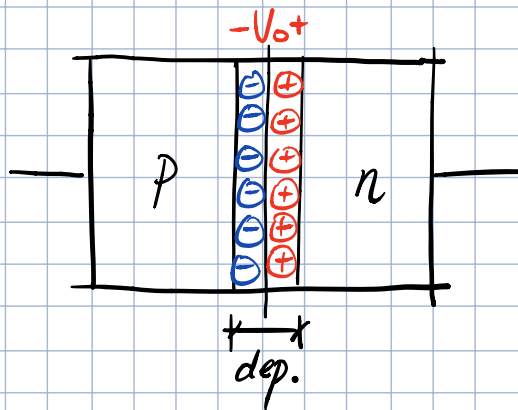
$$I_{\text{Diff}} \rightarrow \leftarrow I_{\text{Drift}}$$



② Reverse Bias.
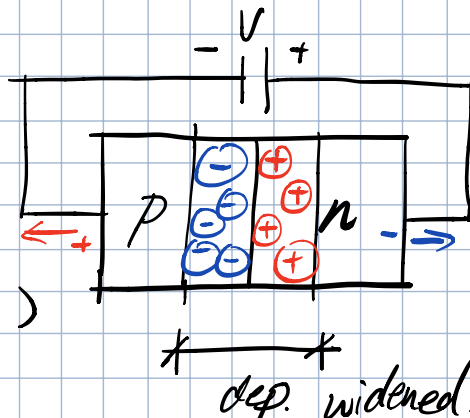
$$I_{\text{Diff}} \rightarrow \leftarrow I_{\text{Drift}} (I_s)$$



③ Forward Bias.

