
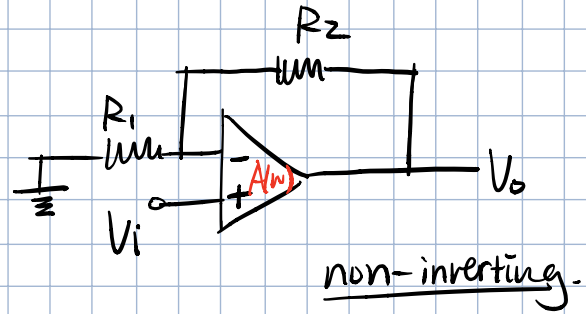
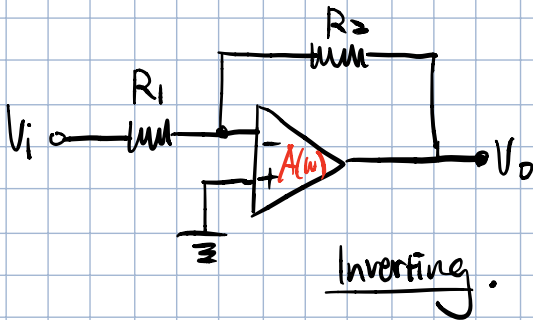


Review Session.


1) Amplifier.

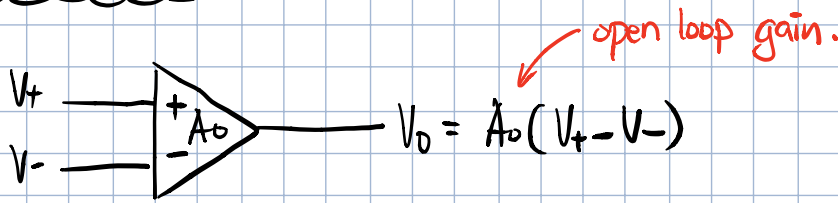

closed loop amplifier.

$$\frac{V_o}{V_i} = \frac{-R_2/R_1}{1 + j\omega/\omega_{3dB}}$$
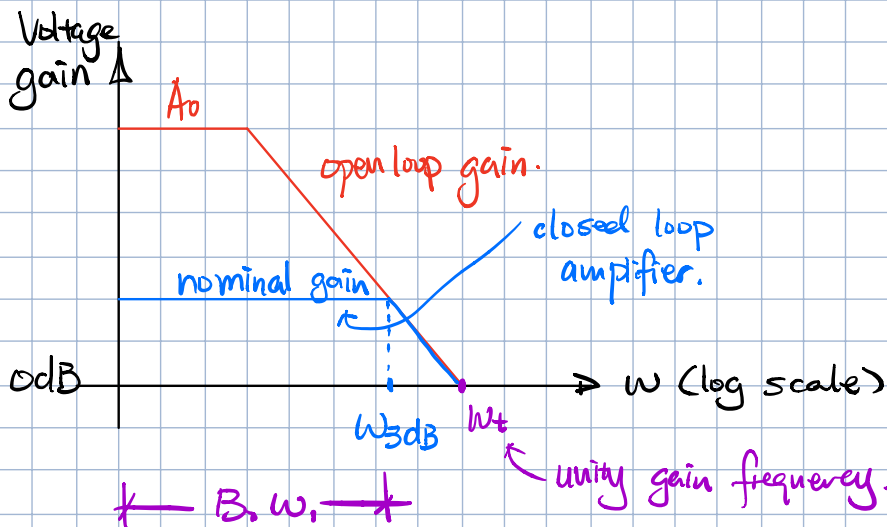
$$\frac{V_o}{V_i} = \frac{1 + R_2/R_1}{1 + j\omega/\omega_{3dB}}$$



$$\omega_{3dB} = \frac{\omega_t}{1 + R_2/R_1}$$

frequency Bandwidth Product


$$(nominal\ gain) (BW) = \omega_t$$

Op Amp limitation.



output voltage saturated. $\approx \pm(V_{CC} - 2V)$

Full power bandwidth: $f_M = \frac{SR}{2\pi V_{O_{max}}}$

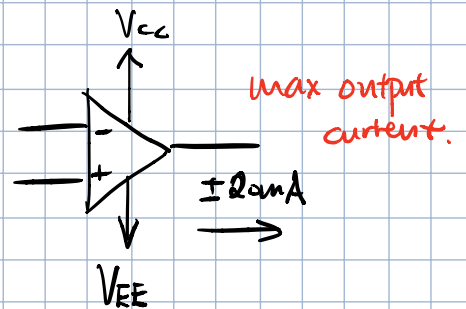max frequency of a sinusoidal waveform. allowed w/o SR limiting effect.



2) Diode

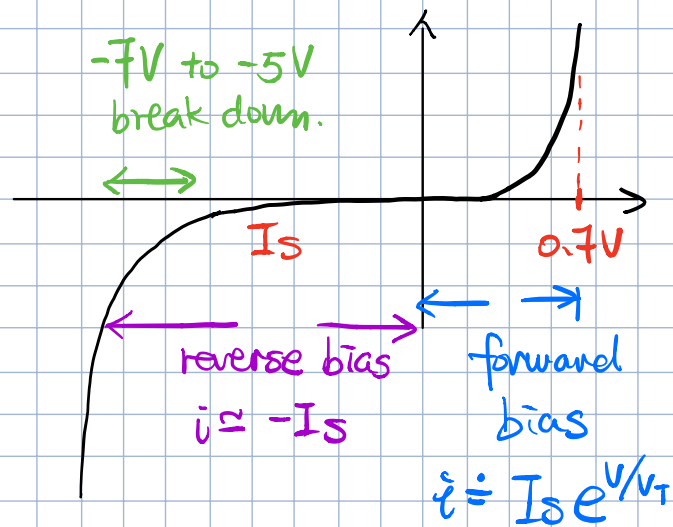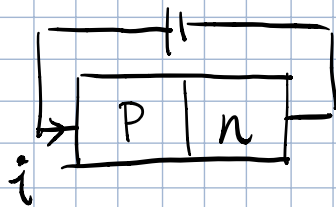

diode small signal model.

$$V_2 - V_1 = V_T \ln \frac{i_2}{i_1}$$

