
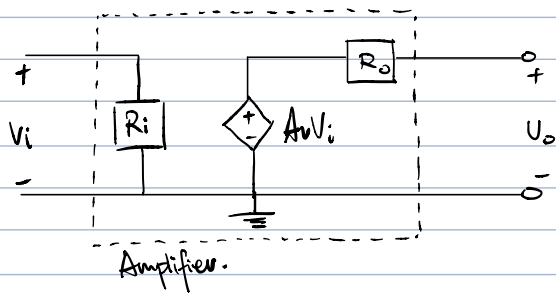



Amplifier.

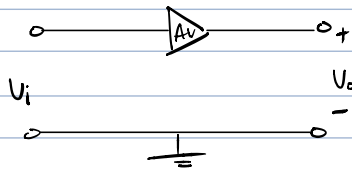

Single-End Style of an Amplifier.



Differential.

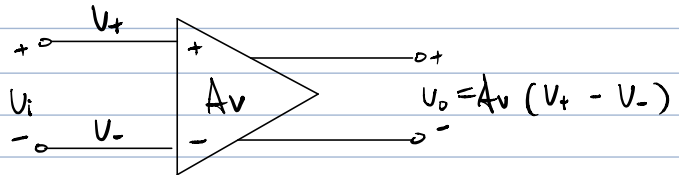

$$\text{gain} = \frac{\text{output}}{\text{input}}$$

voltage gain. = V_o/V_i
(A_v)

current gain. = i_o/i_i
(A_i)

power gain = $\frac{V_o i_o}{V_i i_i} = A_v \cdot A_i$
(A_p)



Decibel (dB)

$$20 \log_{10} |A_v|, \quad 20 \log_{10} |A_i|, \quad 10 \log_{10} |A_p|$$

eg. $A_v = 100$ $20 \log_{10} 100 = 40 \text{ dB}$

$A_v = 1$ $20 \log_{10} 1 = 0 \text{ dB}$

Simple Amplifier.

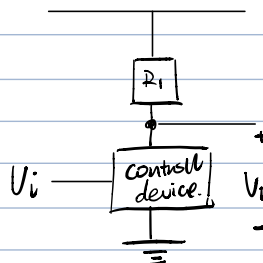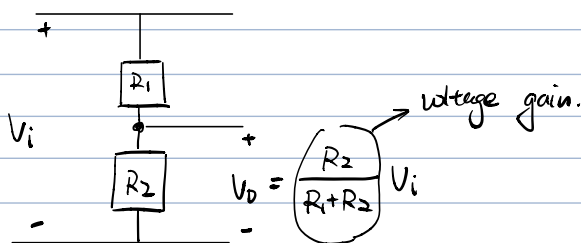




passive amplifier:

- output power \leq input power.

Active Amplifier: (external energy required to achieve)

- output power $>$ input power.

Design.

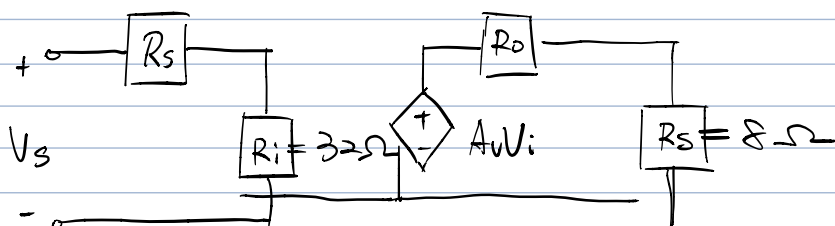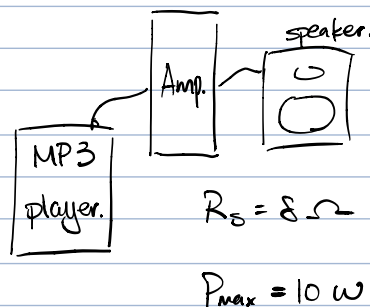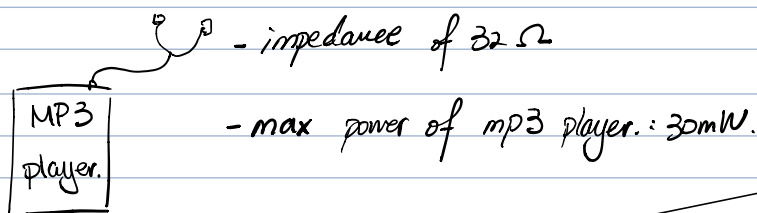


Amplifier Requirement.

$$\text{input power} = \frac{(V_i)^2}{R_i} \quad (30\text{mW}) \quad \rightarrow V_i = \sqrt{(30\text{mW})(32\ \Omega)} = 1\text{ V}$$

$$\text{output power} = \frac{(V_o)^2}{R_s} \quad (10\text{ W}) \quad \rightarrow V_o = \sqrt{(10\text{ W})(8\ \Omega)} = 9\text{ V}$$
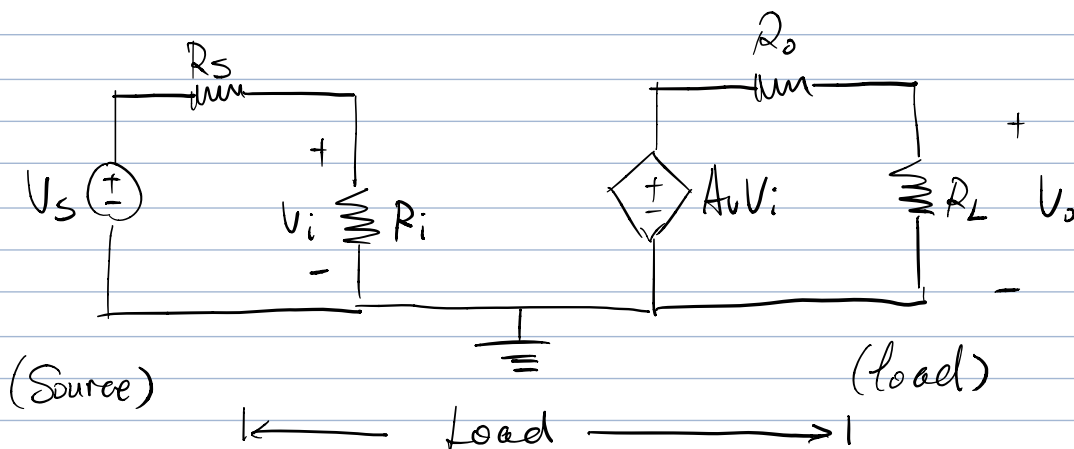
$$\left\{ \begin{array}{l} \text{voltage gain} = 9\text{ V}/1\text{ V} = 9 \\ \text{power gain} = 10\text{ W}/30\text{mW} = 333.3 \\ 10 \log 333.3 = 25\text{ dB} \end{array} \right.$$



$$\frac{V_i}{V_s} = \frac{R_i}{R_s + R_i}$$

$$V_o = A_v V_i \frac{R_L}{R_o + R_L} \Rightarrow \frac{V_o}{V_i} = \frac{R_L}{R_o + R_L} A_v$$

$$\frac{V_o}{V_i} \times \frac{V_i}{V_s} = \frac{V_o}{V_s} = A_v \frac{R_L}{R_o + R_L} \cdot \frac{R_i}{R_s + R_i}$$


Annotations:

- good w/ amplifier. (large) → $\frac{V_o}{V_i} \times \frac{V_i}{V_s}$
- large → A_v
- small → $\frac{R_L}{R_o + R_L}$
- large → $\frac{R_i}{R_s + R_i}$



In Summary:

- large input impedance. (R_i)
- small output impedance. (R_o)
- large gain (A_v)


multi-stage Amplifier.

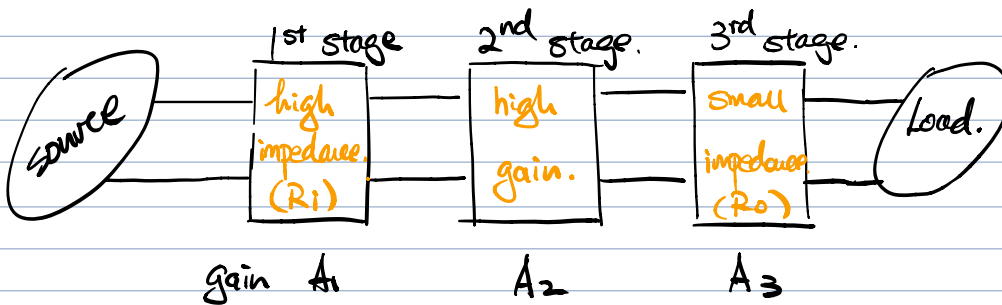

$$\text{overall gain} = A_1 A_2 A_3$$

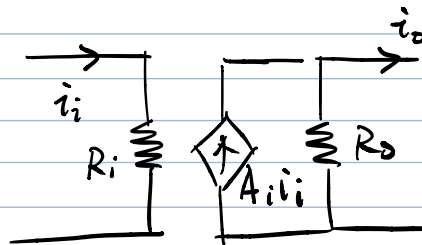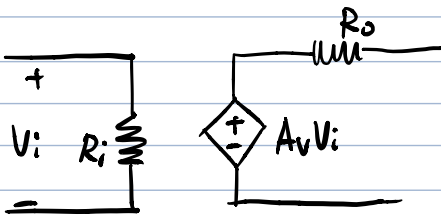

trans conductance.

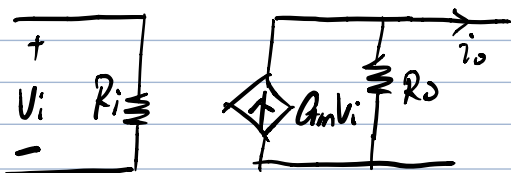

trans Resistance.

