
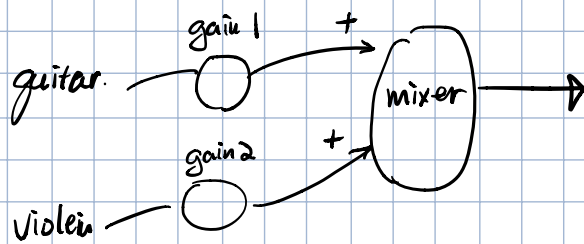


② Adder circuit. (voltage weighted sum)

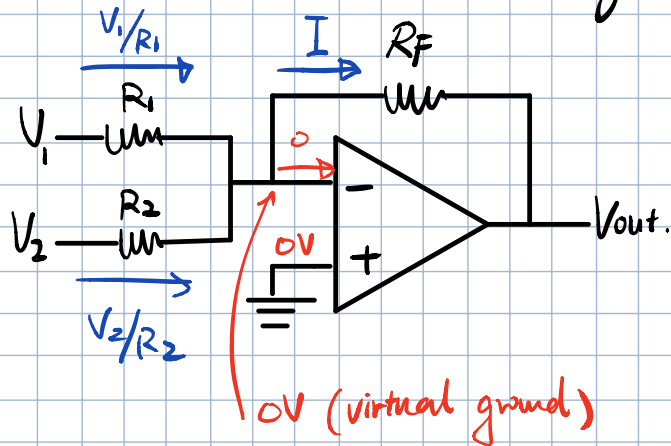

$$I = \frac{V_1}{R_1} + \frac{V_2}{R_2}$$




$$V_{out} = 0 - IR_F$$

$$V_{out} = -\left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2\right) //$$

③ Difference Amplifier.

By Superposition.:

one source @ a time +
sum up results.

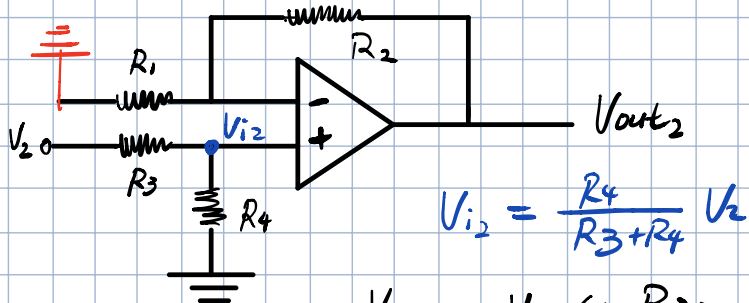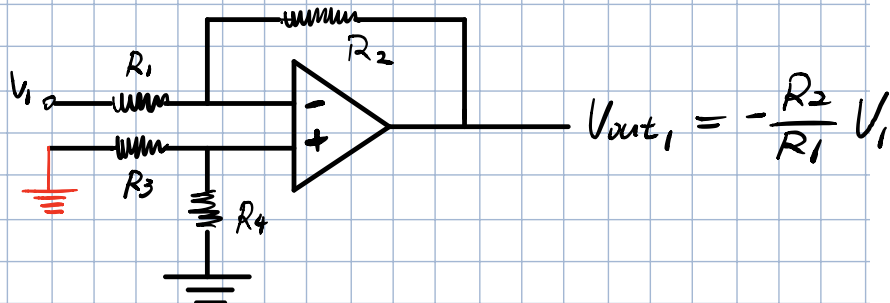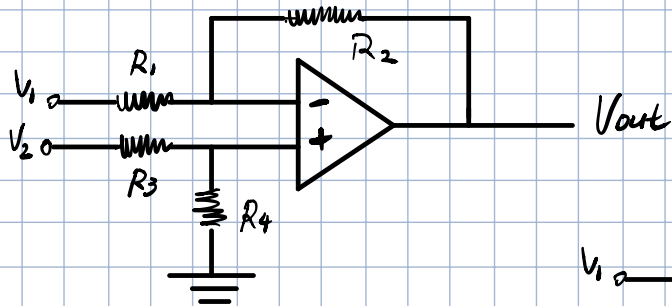

$$V_{i2} = \frac{R_4}{R_3 + R_4} V_2$$

$$V_{out2} = V_{i2} \left(1 + \frac{R_2}{R_1}\right)$$

$$= \frac{R_4}{R_3 + R_4} \left(1 + \frac{R_2}{R_1}\right) V_2$$

$$V_{out} = V_{out1} + V_{out2}$$

$$= -\frac{R_2}{R_1} V_1 + \left(1 + \frac{R_2}{R_1}\right) \frac{R_4}{R_3 + R_4} V_2 //$$

$$\text{if } \frac{R_3}{R_4} = \frac{R_1}{R_2},$$


$$\text{then } V_{out} = \frac{R_2}{R_1} (V_2 - V_1) //$$

drawbacks, very difficult to match.


Resistor value has tolerance.

(mismatch \rightarrow lower input resistance.)

Integrator + Differentiator.

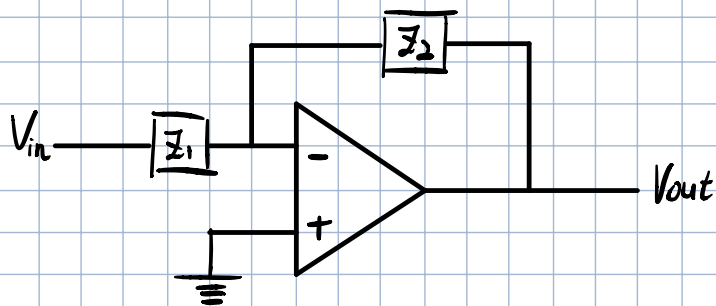

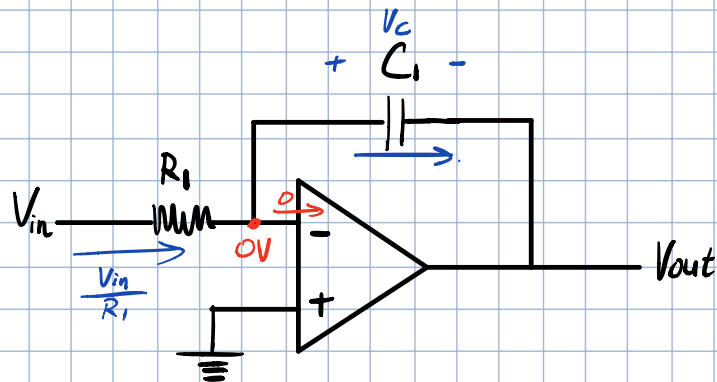
$$\frac{V_{out}}{V_{in}} \approx -\frac{Z_2}{Z_1}$$



$$\frac{V_{out}}{V_{in}} = -\frac{\frac{1}{sC_1}}{R_1} = -\frac{1}{R_1 C_1 s}$$
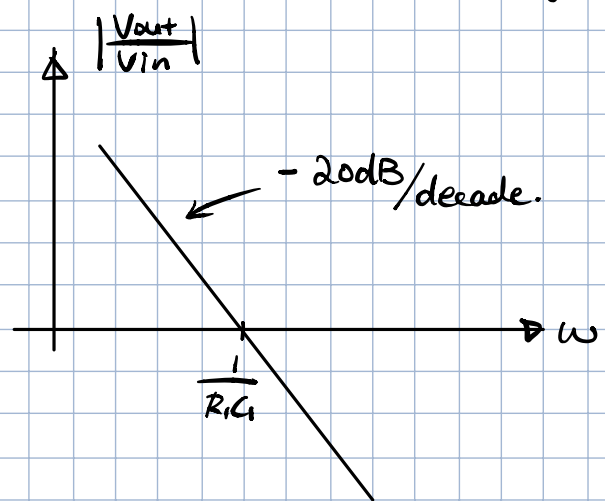
$$s = j\omega, \quad \frac{V_{out}}{V_{in}}(\omega) = -\frac{1}{j\omega R_1 C_1}$$





current through the capacitor.

$$\frac{V_{in}}{R_1} = C \frac{dV_c}{dt}, \quad V_c = 0 - V_{out}$$

$$C \frac{d(-V_{out})}{dt} = \frac{V_{in}}{R_1}$$
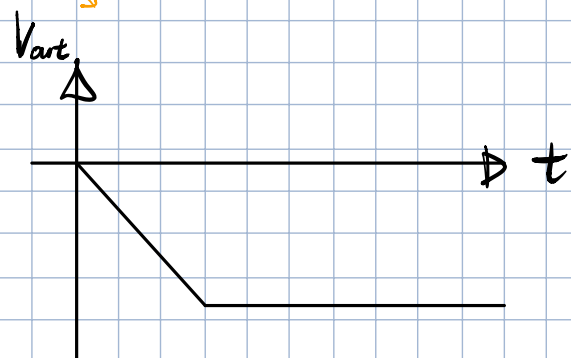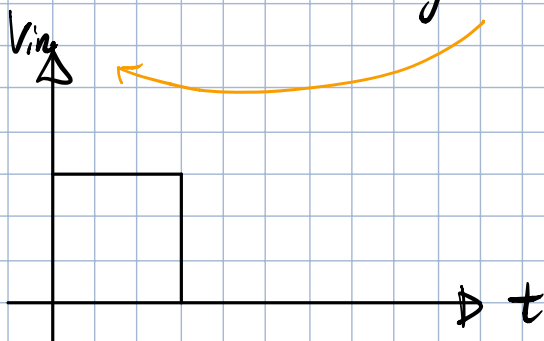
$$V_{out} = -\frac{1}{R_1 C_1} \int V_{in} dt$$



Not working in real circuit, b/c the gain is too high at DC, causing saturation fin.

