

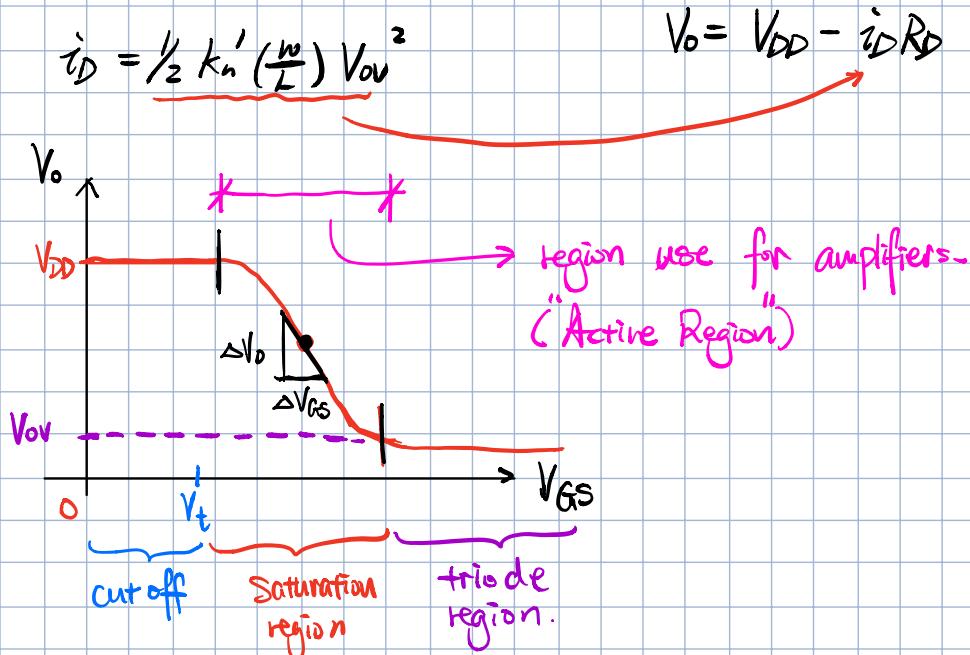
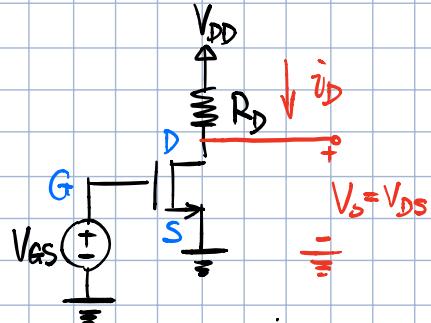
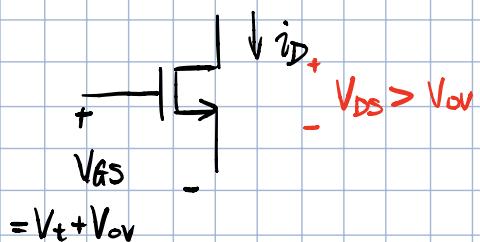


Transistor Amplifiers (MOS, BJT)

NMOS (in Saturation mode)

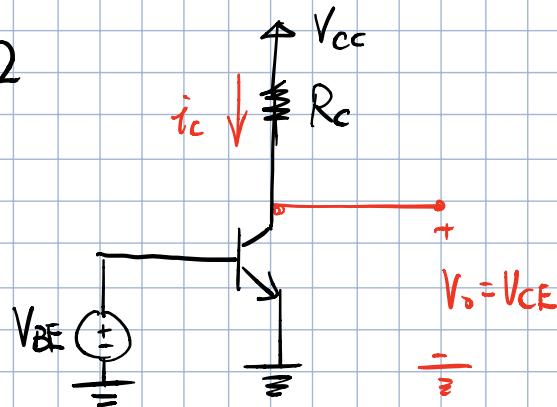



nPN BJT (in Active mode)

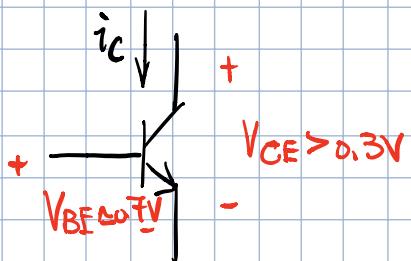


$$i_C = I_s e^{V_{BE}/V_T}$$

$$V_o = V_{CC} - R_C i_C$$

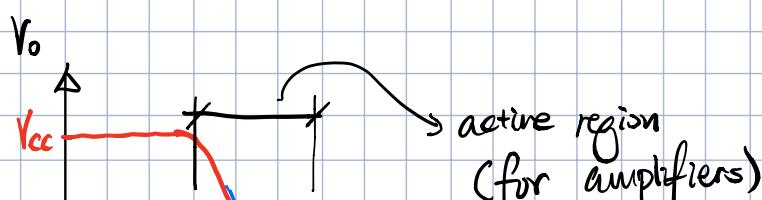

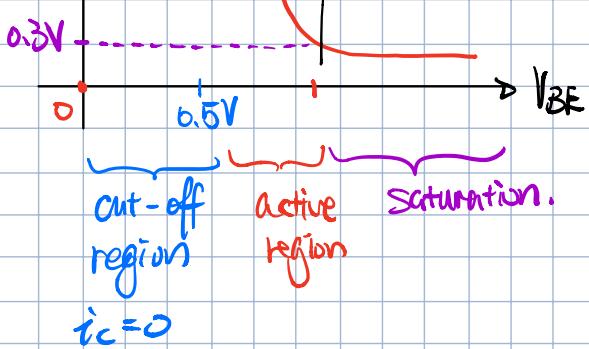

NMOS Amplifier.

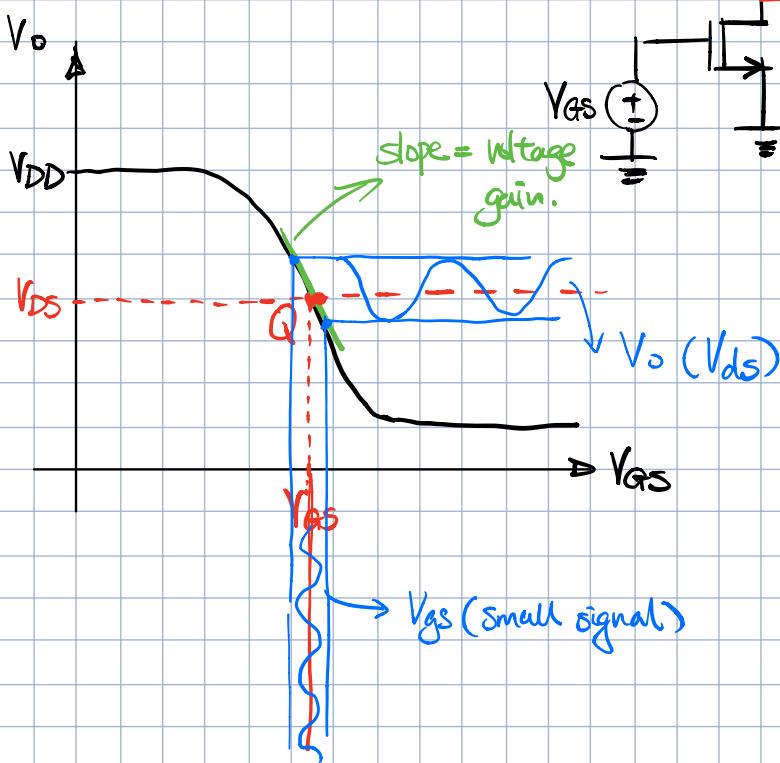

$$\begin{aligned} \text{Total voltage } V_o &= V_{DD} - i_D R_D \\ &= V_{DD} - \left(\frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 \right) R_D \end{aligned}$$

Voltage gain @ the operating point (Q)


$$A_v = \frac{dV_o}{dV_{GS}} \Big|_Q$$

$$= -k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t) R_D$$

$$= -k_n' \left(\frac{W}{L}\right) (V_{GS}) R_D$$

Voltage gain $\propto V_{GS} \propto R_D$
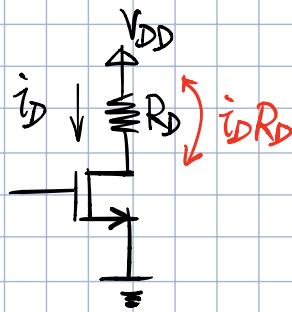
$$A_v = -\frac{\left(k_n' \left(\frac{W}{L}\right) V_{GS}\right) R_D}{2 k_n' V_{GS}} = -\frac{i_D R_D}{V_{GS}}$$




$$2 \cdot \frac{V_{DD}}{2} = I_D$$

maximum value for I_{DRD}
is V_{DD}

maximum voltage gain.

$$|A_v| = \frac{V_{DD}}{V_{GS}/2}$$

Example.

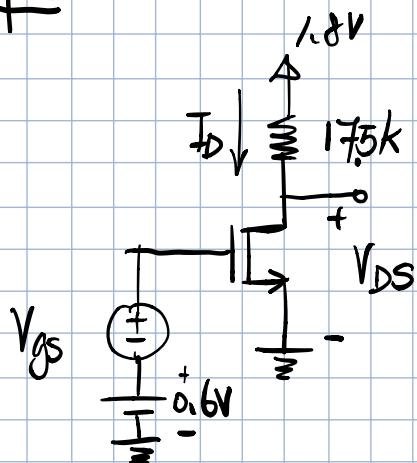

$$V_t = 0.4V \quad k'n' = 0.4mA/V^2, \frac{W}{L} = 10, \lambda = 0$$

a) (DC operation) for $V_{GS} = 0$, find
 V_{DS} , I_D , V_{DS} and A_v

b) (Signal swing) what is the max
allowable V_{GS} ?



$$a) V_{OV} = V_{GS} - V_t = 0.2V$$

$$I_D = \frac{1}{2} k'n' \left(\frac{W}{L} \right) V_{OV}^2 = 0.08mA$$

Eqn for mosfet saturation mode.

$$V_{DS} = 1.8 - 17.5k I_D = 0.4V$$
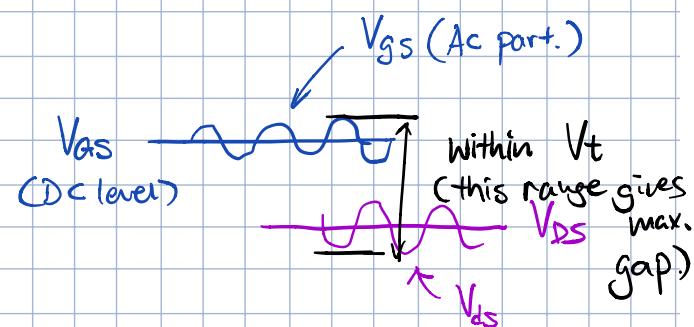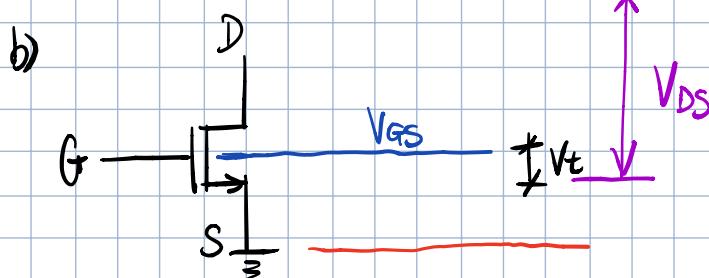
$$A_v = -\frac{I_D R_D}{V_{GS}/2} = -14V/V$$



gate voltage - drain voltage < V_t

cond. for transistor in


Saturation mode.

$$V_{GS} + \hat{V}_{GS} - (V_{DS} - \hat{V}_{DS}) = V_t$$


$$0.6 + \hat{V}_{GS} - (0.4 - 14 \hat{V}_{GS}) = 0.4$$

$$\hookrightarrow |Av| = \hat{V}_{GS} = \hat{V}_{DS}$$
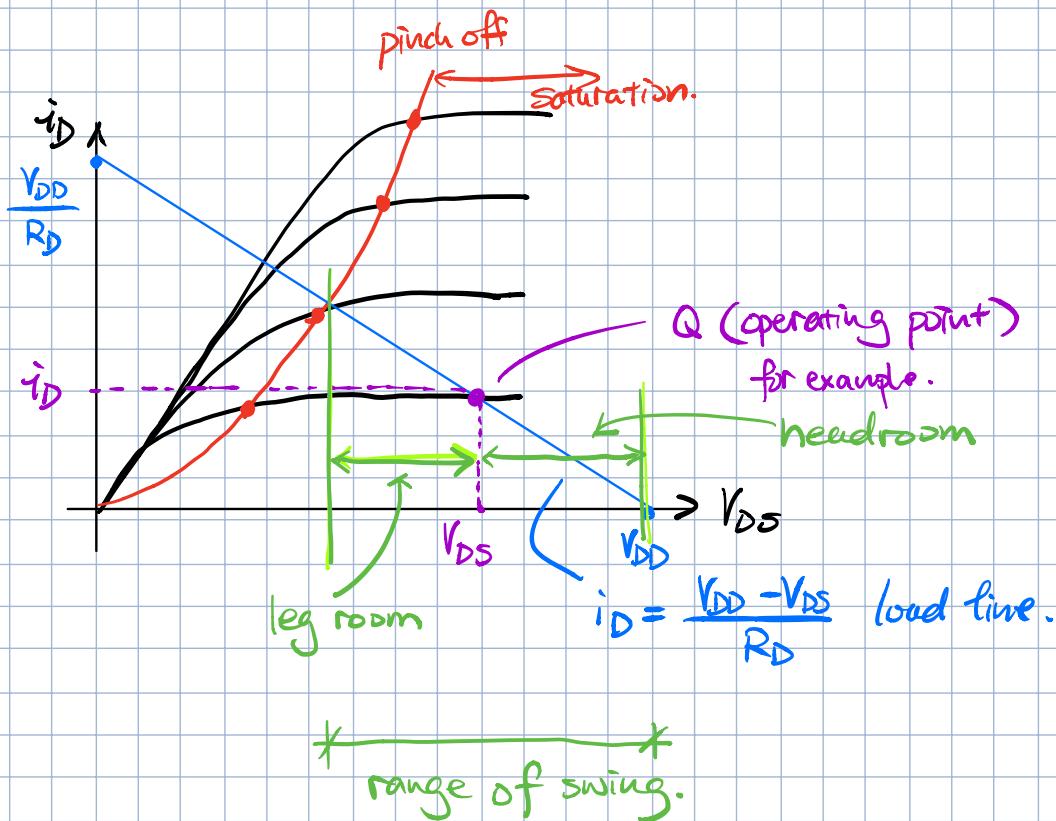
$$\Rightarrow \hat{V}_{GS} = 13.3 \text{ mV} \text{ (max. allowed signal @ the gate)}$$



Small Signal Operation.

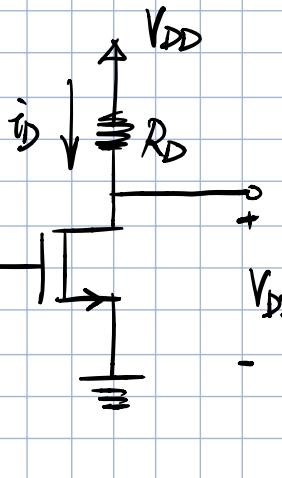

$$i_D = \frac{1}{2} k_n' \left(\frac{w}{l} \right) (V_{GS} - V_t)^2$$

$$= \frac{1}{2} k_n' \left(\frac{w}{l} \right) (V_{GS} + V_{GS} - V_t)^2$$


$$= \frac{1}{2} k_n' \left(\frac{w}{l} \right) (V_{GS} - V_t + V_{GS})^2$$

$$= \frac{1}{2} k_n' \left(\frac{w}{l} \right) (V_{GS} - V_t)^2 \leftarrow \text{DC component}$$

If $V_{gs} \ll 2V_{or}$, we can drop this distortion term $\rightarrow + \frac{1}{2} k_n' \left(\frac{w}{l}\right) V_{gs}^2 \leftarrow$ non-linear distortion.

$$i_D \approx I_D + i_d$$
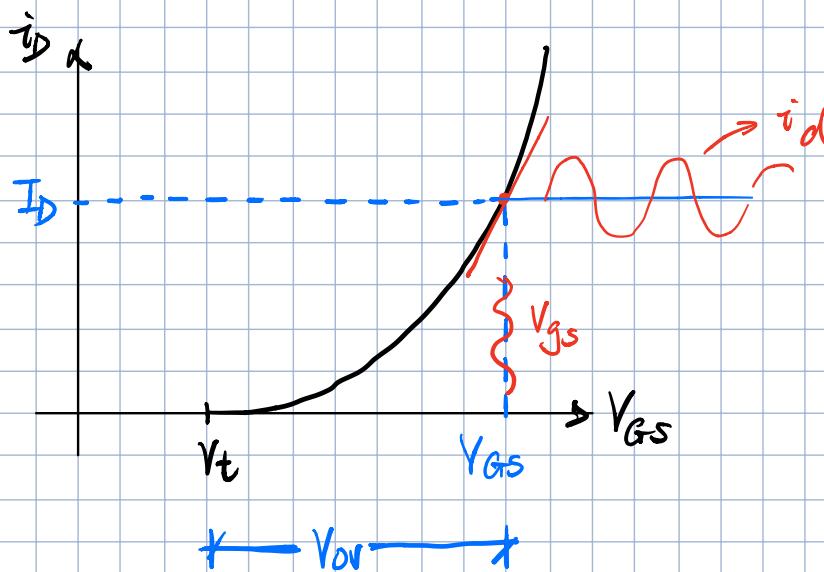
$$I_D = \frac{1}{2} k n' \left(\frac{w}{L} \right) (V_{GS} - V_t)^2$$



$$i_d = k_n' \left(\frac{w}{L} \right) (V_{GS} - V_T) V_{GS}$$

IAS


1

$$\frac{1}{\text{resistance}} \left(\frac{1}{\Omega} \right)$$


("gm" trans-conductance.)

$$i_d = g m \sqrt{g s}$$


Small Signal model.

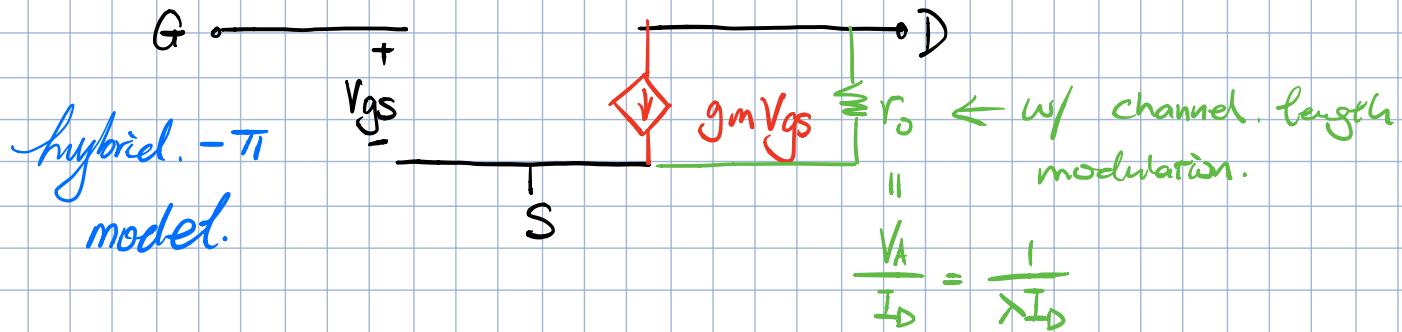

Summary :

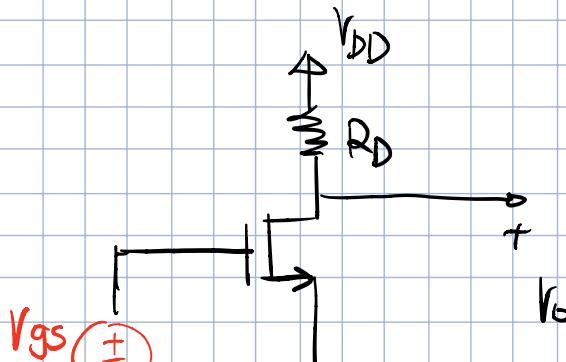

1) DC Analysis.

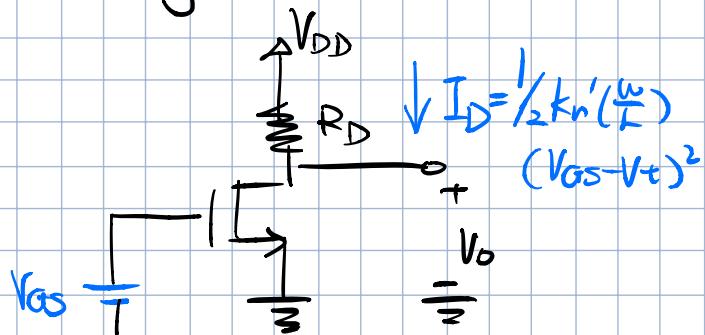


$$\frac{V_{GS}}{I}$$

$$\frac{1}{m}$$

$$\frac{1}{g_m}$$

2) Calculate parameter used in small signal model

3) Build small signal model.

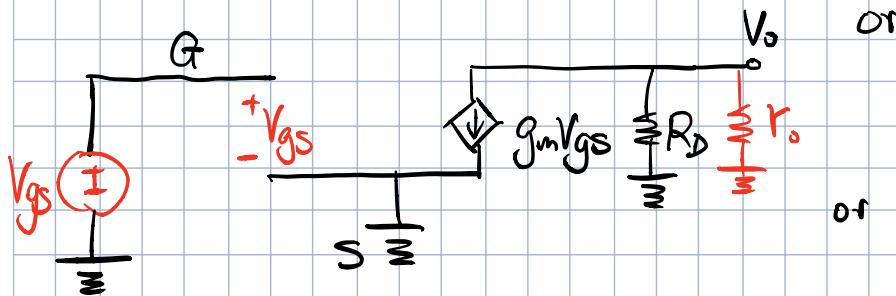

$$g_m = k_n \left(\frac{W}{L} \right) V_{BV}$$

$$g_m = \sqrt{2k_n \frac{W}{L} I_D}$$

$$g_m = \frac{2I_D}{V_{BV}}$$

$$V_o = -g_m V_{GS} \quad (R_D \parallel r_o), \text{ voltage gain } \frac{V_o}{V_{GS}} = -g_m (R_D \parallel r_o)$$