
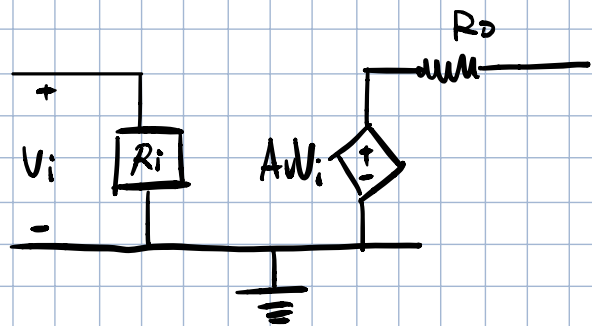




Ideal Op-amp circuits.


Operational Amplifier. (op-amp)

	Ideal amplifier.	741	modern IC op-amp.
A_o	∞	100,000	50 - 100
Input Impedance.	∞	few $M\Omega$	few $M\Omega$
Output Impedance.	0	< 100 Ω	few $k\Omega$
BW.	∞	15 MHz	few GHz
power diss.	0	80 mW	5-10 mW
cost.	0	< \$1	\$ 10^{-5}

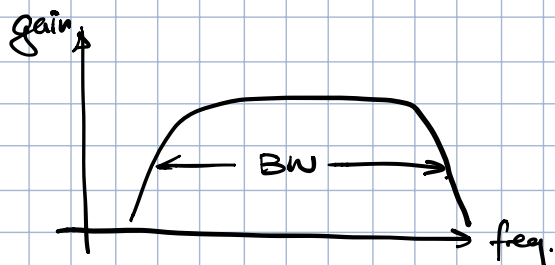


Op-Amp Basics:

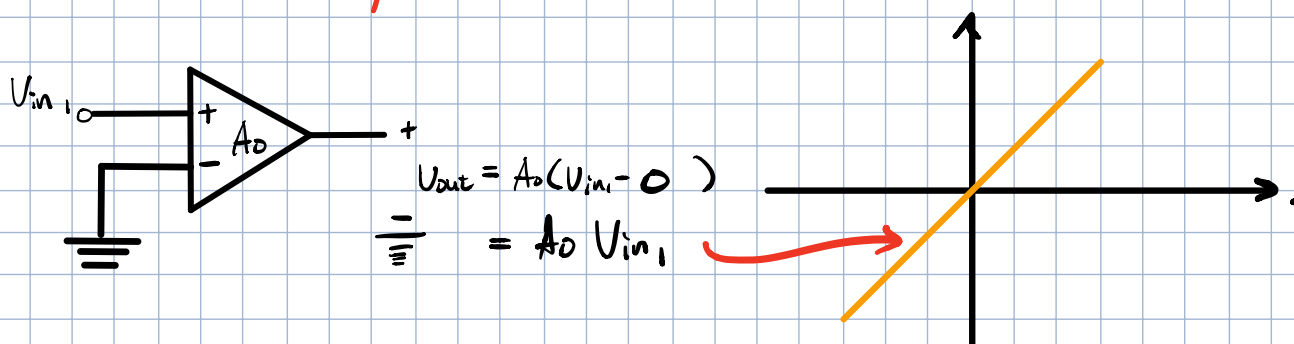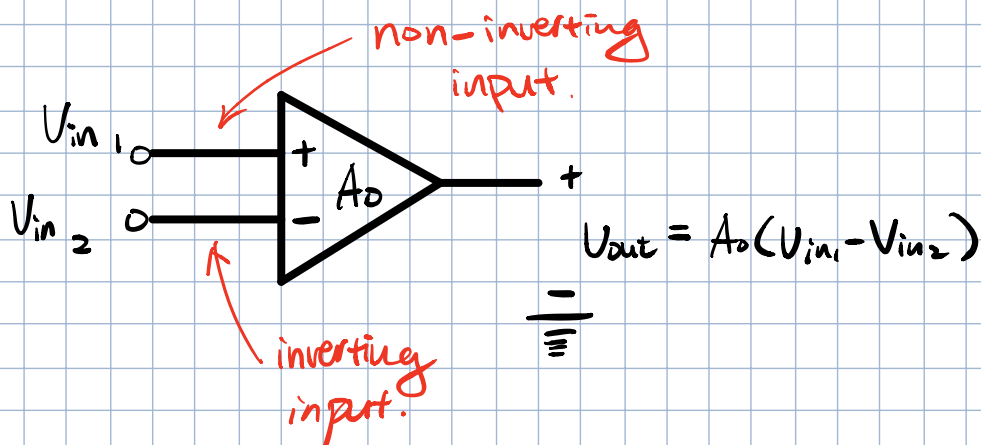

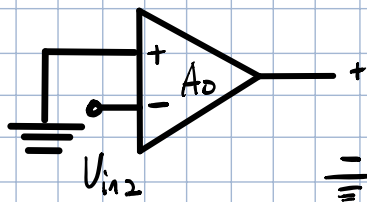


$$V_{out} = A_o(0 - V_{in2})$$

$$= -A_o V_{in2}$$

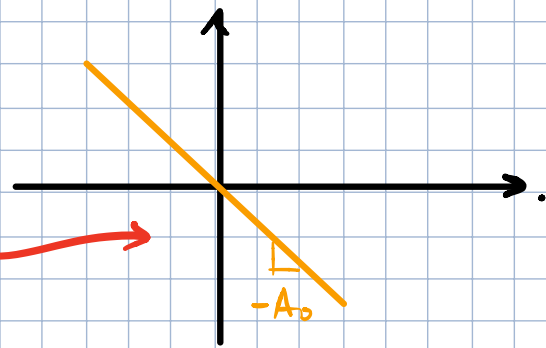

non-inverting amplifier.

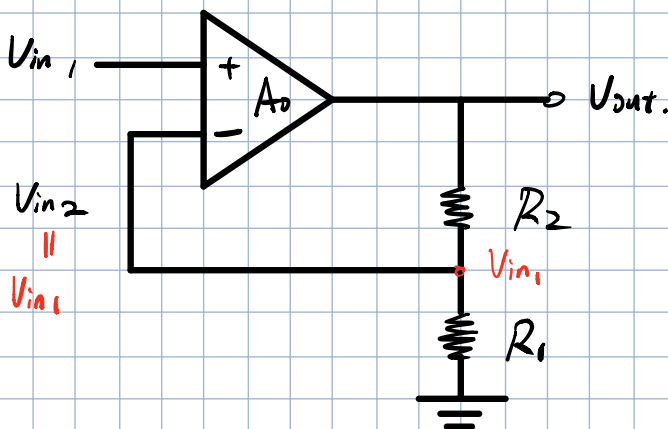


Case 1: $A_o \rightarrow \infty$

$$V_{out} = A_o(V_{in1} - V_{in2})$$

finite # \rightarrow i.e. $V_{in1} \parallel V_{in2}$

$$V_{in1} = \frac{R_1}{R_1 + R_2} V_{out} \rightarrow \frac{V_{out}}{V_{in}} \approx \frac{R_1 + R_2}{R_1}$$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_2}{R_1}$$

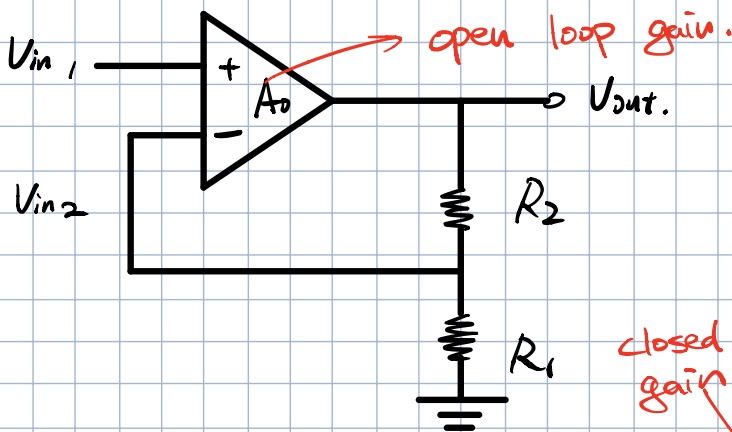

Case 2: $A_o \neq \infty$

$$V_{in2} = \frac{R_1}{R_1 + R_2} V_{out}$$

$$V_{out} = A_o(V_{in1} - V_{in2})$$

$$= A_o(V_{in1} - \frac{R_1}{R_1 + R_2} V_{out})$$

$$\frac{V_{out}}{V_{in}} = \frac{A_o}{1 + \frac{R_1}{R_1 + R_2} A_o} = \frac{1 + \frac{R_2}{R_1}}{1 + (1 + \frac{R_2}{R_1}) / A_o}$$

if $A_o \rightarrow \infty$,


$$\frac{V_{out}}{V_{in}} \approx 1 + \frac{R_2}{R_1} \quad (\text{Agrees w/ previous})$$

(closed loop gain in this case is independent of A_o)

Inverting Amplifier.

Case 1: $A_o \rightarrow \infty$

$\frac{V_{in} - 0}{R_1}$

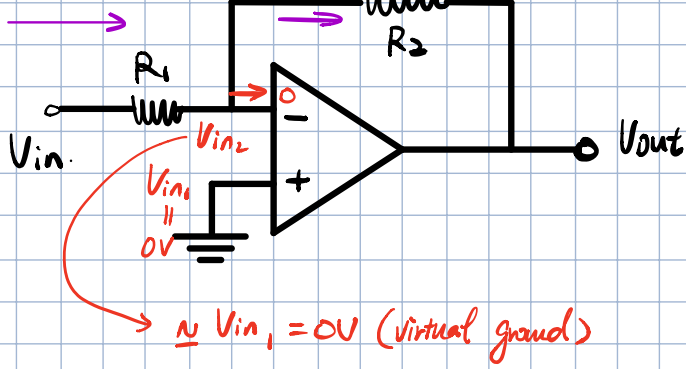


$$V_{out} = A_o (V_{in1} - V_{in2})$$

\downarrow bounded $\downarrow \infty$ $V_{in1} \approx V_{in2}$

$$V_{out} = 0 - \frac{V_{in}}{R_1} R_2$$

$$\frac{V_{out}}{V_{in}} \approx - \frac{R_2}{R_1}$$

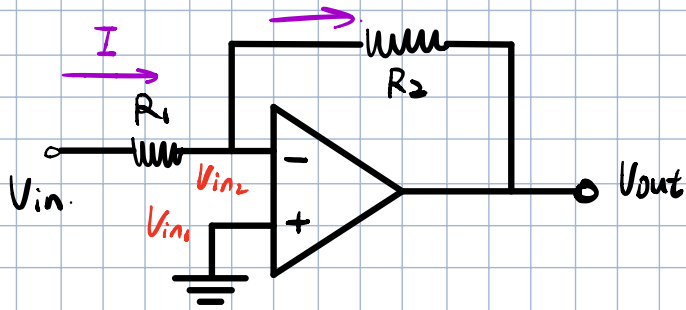

Case 2: $A_o \neq \infty$

$$V_{out} = A_o (V_{in1} - V_{in2})$$

$$= A_o (0 - V_{in2})$$


$$V_{in2} = - \frac{V_{out}}{A_o}$$

$$I = \frac{V_{in} - V_{in2}}{R_1} = \frac{V_{in} + \frac{V_{out}}{A_o}}{R_1}$$

$$V_{out} = V_{in2} - I R_2 \rightarrow \frac{V_{out}}{V_{in}} = \frac{-R_2/R_1}{1 + (1+R_2/R_1)/A_o}$$


Application of the two basic configurations.


① Unity gain buffer.

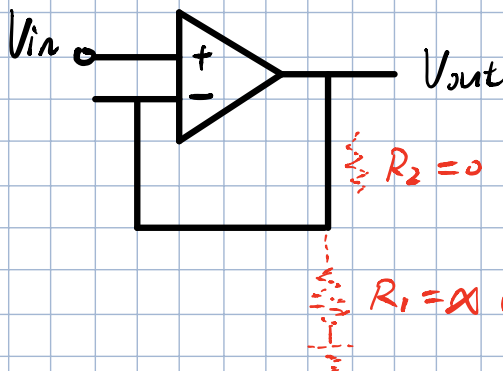

$$\frac{V_{out}}{V_{in}} = \approx 1 + \frac{R_2}{R_1} \approx 1$$

$\nearrow \infty$

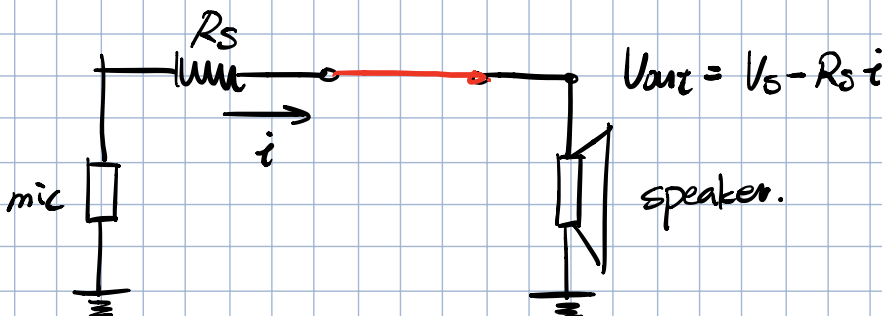

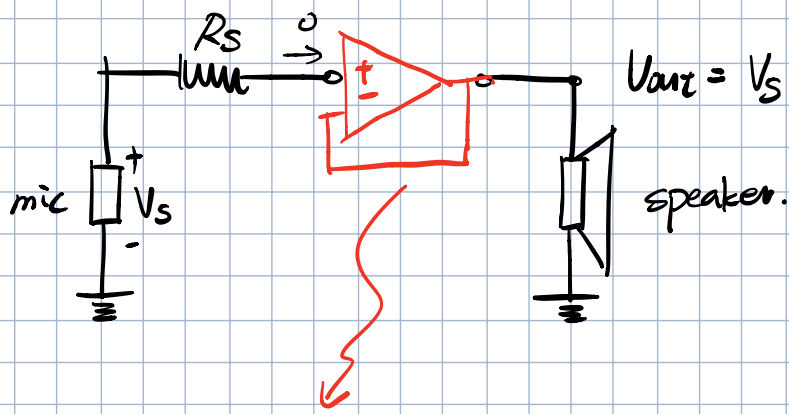

A buffer has high input impedance, which let the circuit sense (detect) voltage w/o loading the circuit.