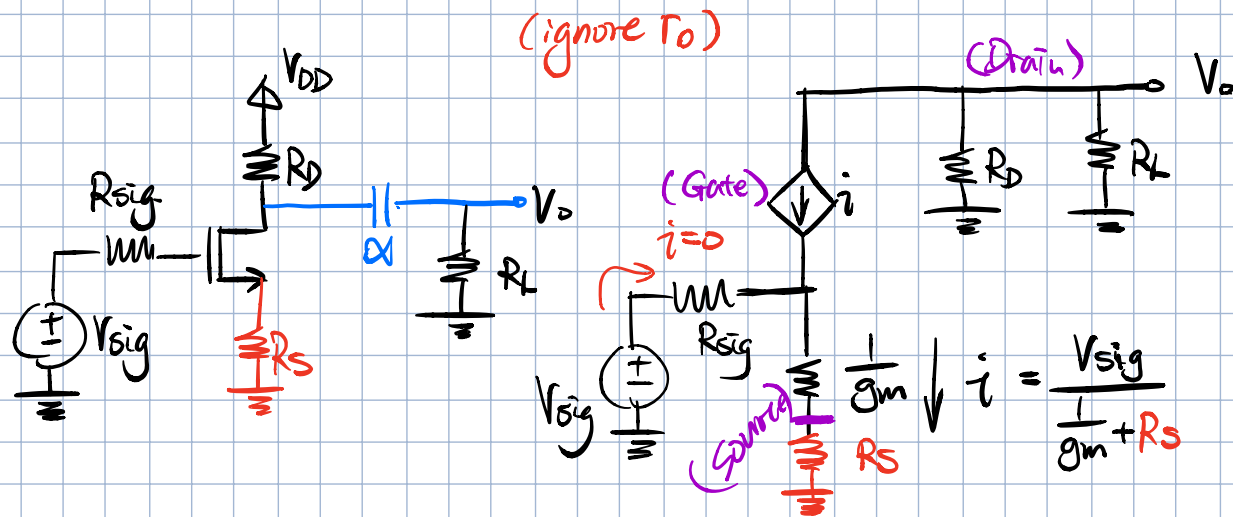






CS but with a source resistance (R_s)



$$V_o = -i(R_D || R_L) = -\frac{V_{sig}}{\frac{1}{g_m} + R_s} (R_D || R_L)$$


$$\text{gain} = \frac{V_o}{V_{sig}} = -\frac{R_D || R_L}{\frac{1}{g_m} + R_s} \quad \text{reduces the voltage gain.}$$

$$\text{if } R_s \gg \frac{1}{g_m}, \text{ gain} \approx -\frac{R_D || R_L}{R_s}$$

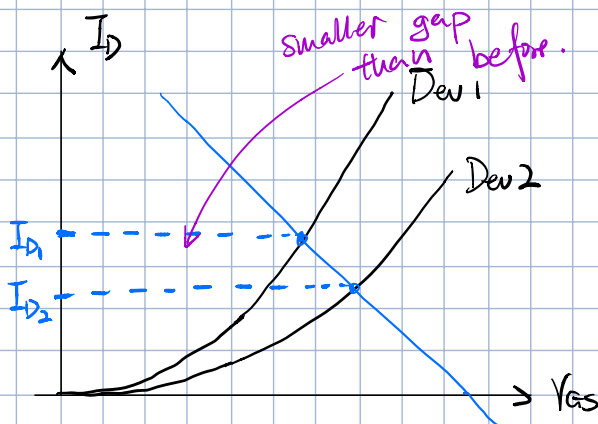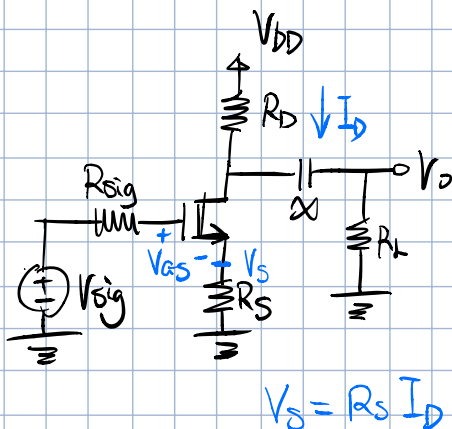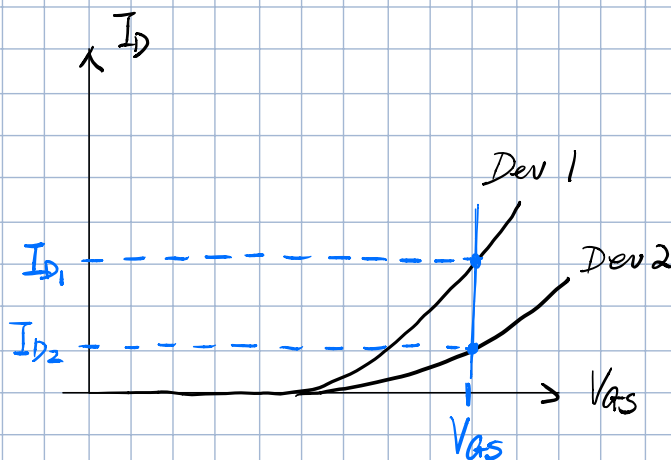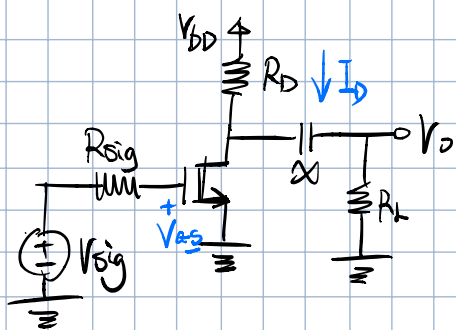

$$V_{GS} = V_{sig} - R_S I_D, \quad I_D \propto (V_{GS} - V_t)^2$$

Common Emitter (CE)

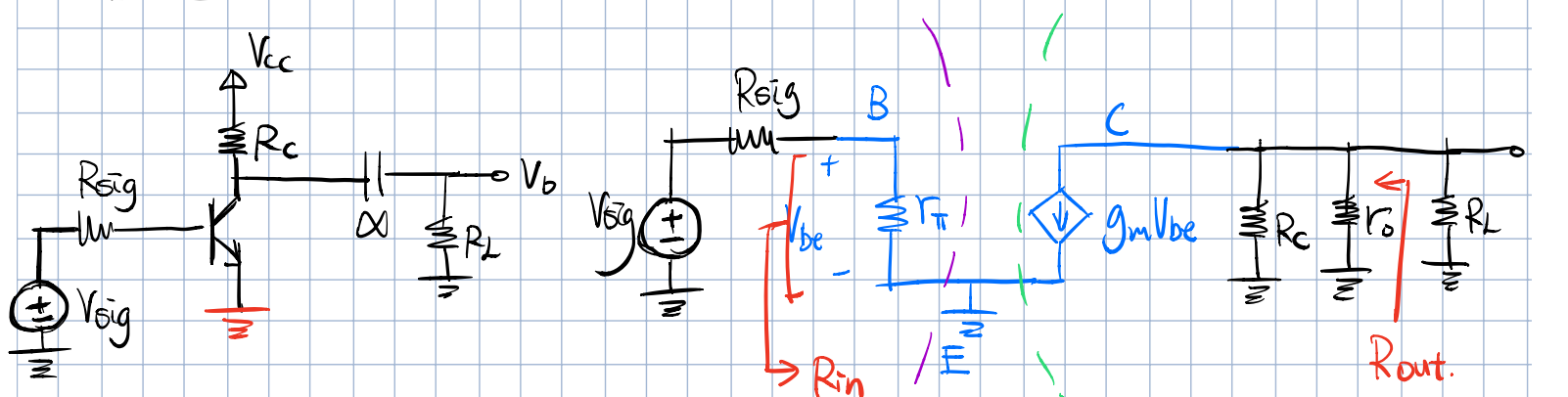

$$V_{be} = \frac{r_{\pi}}{R_{sig} + r_{\pi}} V_{sig}$$

$$V_o = -g_m V_{be} (R_c \parallel r_o \parallel R_L)$$

$$\frac{V_{be}}{V_{sig}} = \frac{r_{\pi}}{R_{sig} + r_{\pi}}$$

$$\frac{V_o}{V_{be}} = -g_m (R_c \parallel r_o \parallel R_L)$$

$$\text{Voltage gain} = \frac{V_o}{V_{sig}} = -g_m \frac{r_{\pi}}{R_{sig} + r_{\pi}} (R_c \parallel r_o \parallel R_L)$$


$$\frac{V_o}{V_{sig}} = -\beta \frac{R_c \parallel r_o \parallel R_L}{R_{sig} + r_{\pi}}$$

\uparrow resistance in collector
 \uparrow resistance in the base.

input resistance $R_{in} = r_{\pi}$

output resistance. $R_{out} = R_c \parallel r_o$

CE with RE (ignore r_o)

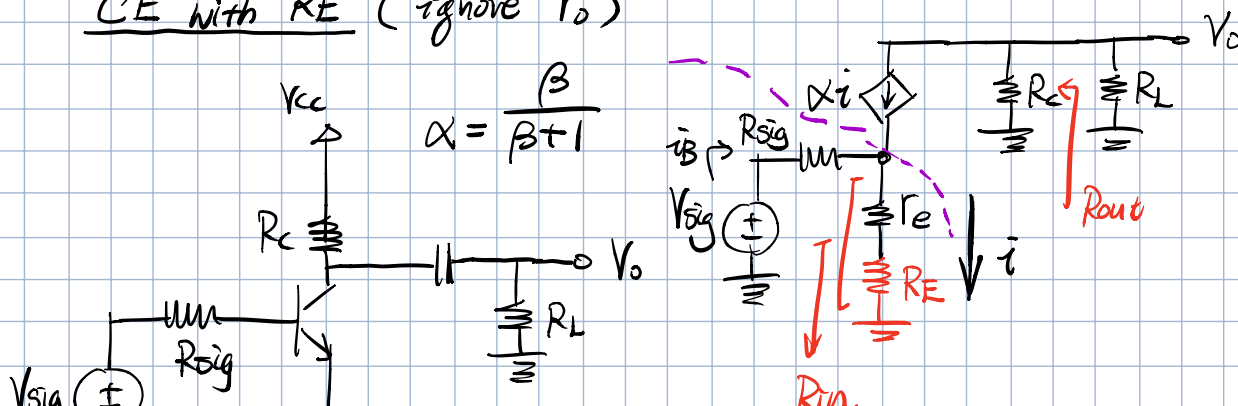

$$R_{in} = (\beta + 1)(r_e + R_E)$$

reflection rule

$$i_B = \frac{V_{sig}}{R_{sig} + R_{in}}$$

$$i = (\beta + 1)i_B = (\beta + 1) \frac{V_{sig}}{R_{sig} + R_{in}}$$

$$V_o = -\alpha i (R_C \parallel R_L)$$

$$= -\alpha (\beta + 1) \frac{V_{sig}}{R_{sig} + R_{in}} (R_C \parallel R_L)$$

$$\text{gain} = \frac{V_o}{V_{sig}} = -\alpha (\beta + 1) \frac{R_C \parallel R_L}{R_{sig} + R_{in}}$$

$$= -\beta \frac{R_C \parallel R_L}{R_{sig} + (\beta + 1)(r_e + R_E)}$$

resistance in collector.

resistance in base.