

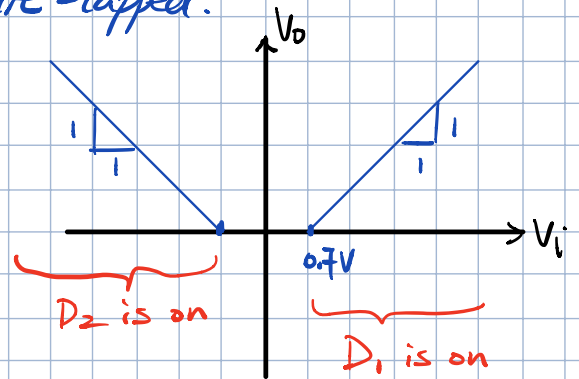
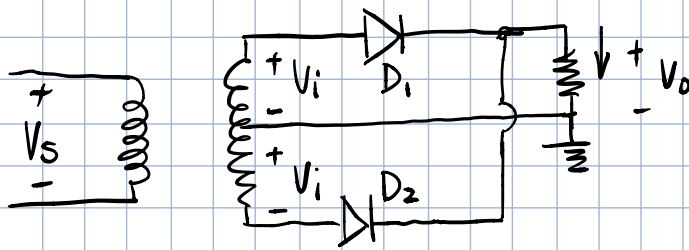
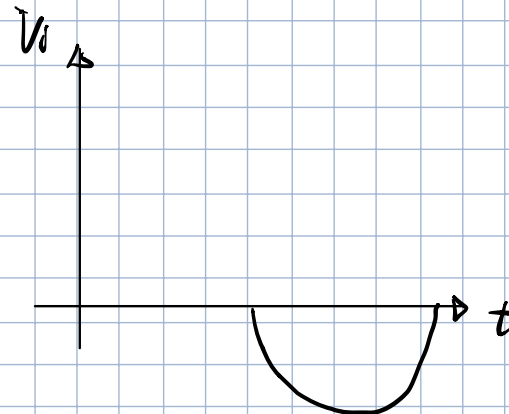
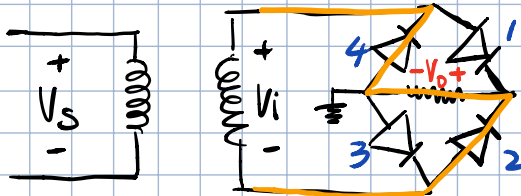


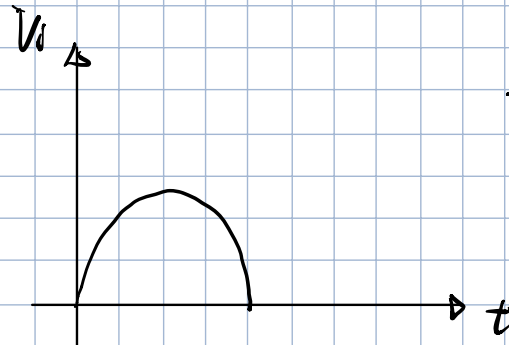full wave rectifier w/ capacitor. centre-tapped.



V_i -ve cycle. V_i +ve cycle.


Bridge rectifier: (F.W.R)

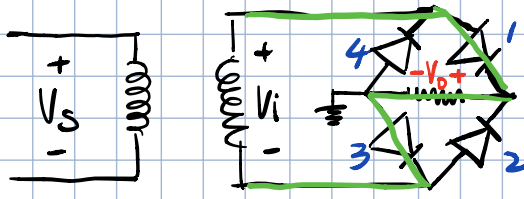


D_1, D_3 ON
 D_2, D_4 OFF

D_1, D_3 OFF
 D_2, D_4 ON

Bridge rectifier. w/ capacitor.

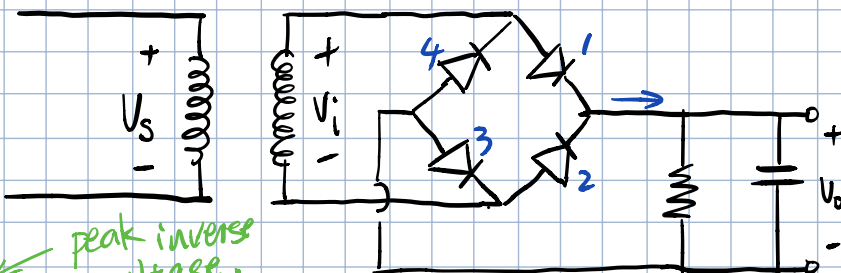

PIV ← peak inverse voltage.
2x0.7

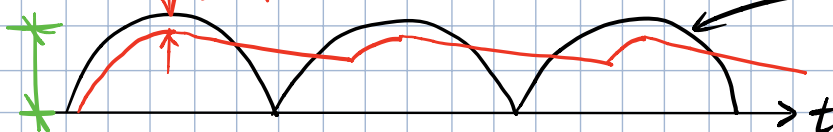

discharging

w/o capacitor.

Compare to H.W.R. discharge time $\approx T/2$ hence the ripple is reduced.

for H.W.R: $V_r \doteq \frac{V_p - 0.7}{fRC}$

for F.W.R: $V_r \doteq \frac{V_p - 0.7 \times 2}{2fRC}$


$i_{Dmax} = i_L (1 + 2\pi \sqrt{\frac{V_p}{V_r}})$

$i_{Dmax} = i_L (1 + 2\pi \sqrt{\frac{V_p}{2V_r}})$





Design a unit that operates from a supply of 240V AC @ 50Hz.

The unit is required to drive an appliance of a fairly constant input of 12V and takes a current in the range of 100mA to 200mA.

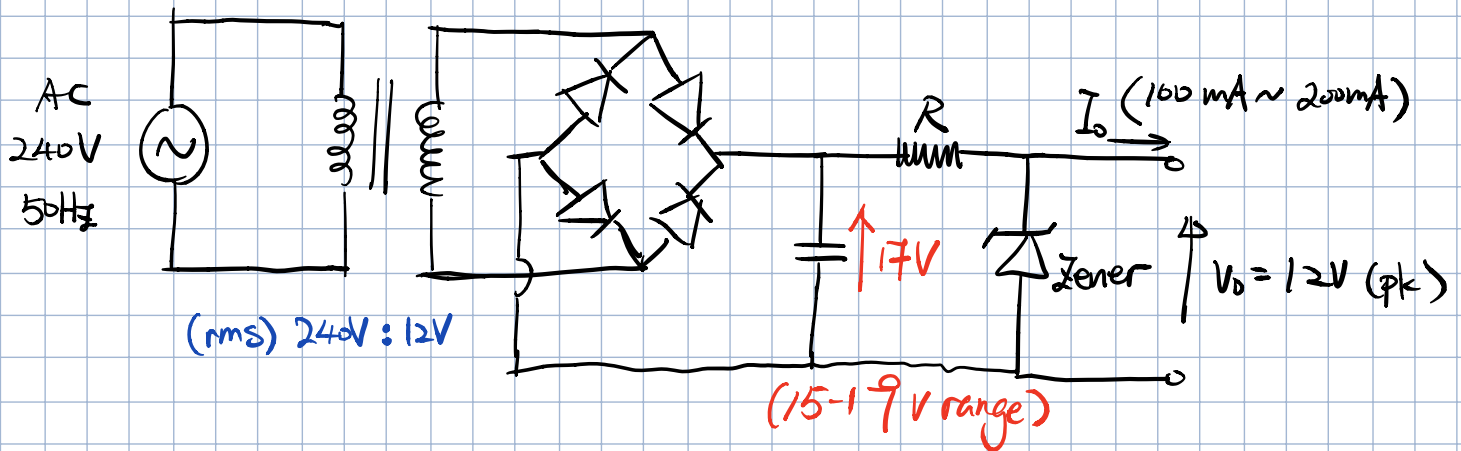1) AC to DC conversion. 2) Voltage step down.



Aside: Zener diode.

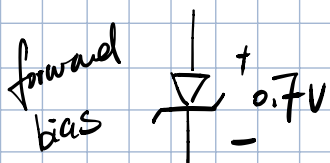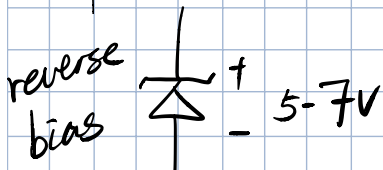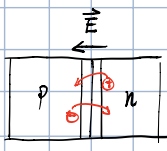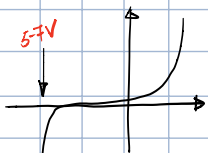

$17V_{pk} \rightarrow 12V_{rms} = \frac{17}{\sqrt{2}} V$

$R = \frac{(15V - 12V)}{(200mA)} = 15\Omega$
 (lowest voltage) (highest current)

$P_R = \frac{V^2}{R} = \frac{(19-12)^2}{15} = 3.3W$

$P_{Zener} = VI = 12V \times \left(\frac{(19-12)}{15}\right) = 5.6W$
 ← max. possible current going through the diode.