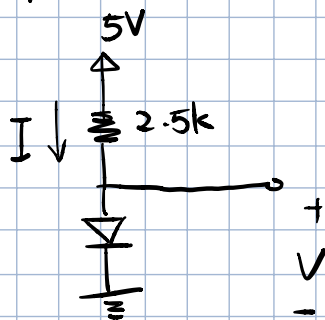


Example.




1) Ideal diode model ($V_D = 0$ when conducting)

$$\text{diode on: } V = 0V, I = \frac{5-0}{2.5k} = 2mA$$

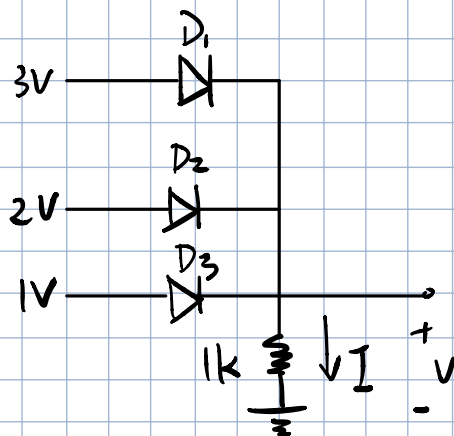2) Diode CVD model ($V_D = 0.7V$ when conducting)

$$\text{diode on: } V = 0.7V, I = \frac{5-0.7}{2.5k} = 1.72mA$$




1) ideal diode. (D_1 on, $D_2 \neq D_3$ off)

$$V = 3V, I = \frac{3}{1k} = 3mA$$

2) CVD model (D_1 on, $D_2 \neq D_3$ off)

$$V = 3V, I = \frac{3-0.7}{1k} = 2.3mA$$


Diode Exponential Model.

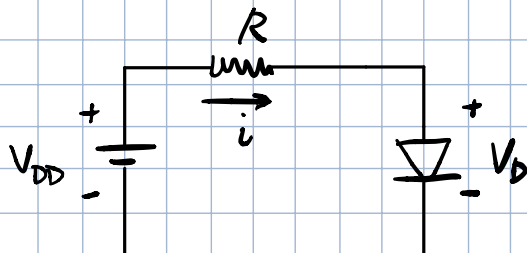

$$\text{diode eqn.: } i = I_s e^{V_D/V_T} \leftarrow 26mV$$

cct eqn.: (KVL)
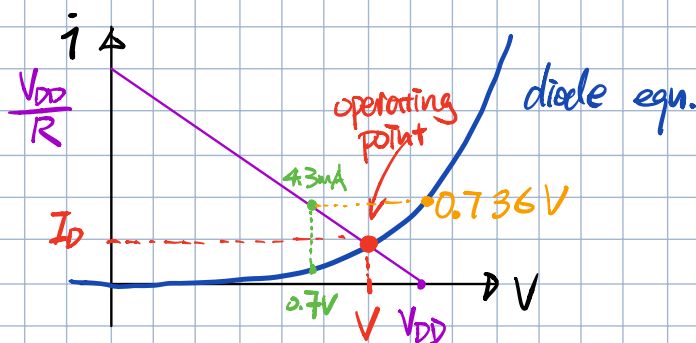
$$-V_{DD} + Ri + V_D = 0, \quad i = \frac{V_{DD} - V_D}{R}$$



Solve by iteration starting w/ some given value.

i.e. $V_{DD} = 5V$, $R = 1k\Omega$, diode has $0.7V$ at $1mA$

1st iteration: $V_D = 0.7V$

$$\text{load eqn. } I_D = \frac{V_{DD} - V_D}{R} = \frac{5 - 0.7}{1k} = \underline{4.3mA} \quad \text{new } I_D$$

$$\text{diode eqn. } V_2 - V_1 = V_T \ln \frac{I_2}{I_1}$$

$$V_2 = V_1 + V_T \ln \frac{I_2}{I_1} = 0.7 + (25mV) \ln \frac{4.3mA}{1mA} \\ = \underline{0.736V} \quad \text{new } V_D$$

2nd iteration: $V_D = 0.736V$


$$\text{load eqn. } I_D = \frac{V_{DD} - V_D}{R} = \frac{5 - 0.736}{1k} = \underline{4.264mA} \quad \text{new } I_D$$

$$\text{diode eqn. } V_2 = V_1 + V_T \ln \frac{I_2}{I_1} = 0.736 + (25mV) \ln \frac{4.264}{4.3} \\ = \underline{0.736V} \quad \text{new } V_D$$

not much change in value V_D or I_D , we stop iteration.

⇒ Operation pt. is $(I_D, V_D) = (4.264mA, 0.736V)$

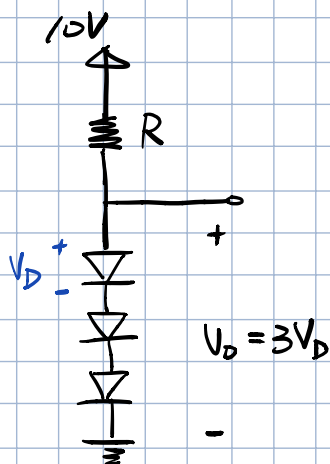example. Design the ckt to have an open ckt voltage of 2.4V assume that the diode are 0.7V @ 1mA



we want each diode to have 0.8V

→ find the current required. (i)

→ calculate the resistance (R)

$$\text{diode eqn. } i = I_S e^{V_D/V_T}$$

$$V_2 - V_1 = V_T \ln \frac{I_2}{I_1}$$

$$0.8 - 0.7 = (25mV) \ln \frac{I_2}{I_1}$$

$$\Rightarrow I_2 = 54.6 \text{ mA}$$

$$\text{load eqn.: } R = \frac{10 - V_0}{i} = \frac{10 - 2.4}{54.6 \text{ mA}}$$

$$R = 139 \Omega$$

Small Signal diode model.

